

**The University of Portland
Donald P. Shiley School of Engineering**

**EE352
Electronic Circuits II
HOMEWORK 2**

Assigned: Fri, Jan 24, 2020
Due: Mon, Feb 3, 2020

Problems:

1. For the active-loaded BJT Differential Amplifier on the next page, assume the BJT's are matched and have the following model parameters: $\beta_n=150$, $\beta_p=100$, $V_{An}=130V$, $V_{Ap}=80V$, $V_T=25mV$, and $V_{BE-on}=0.7V$ (for all BJT's).
 - a) Determine the DC node voltages (except the output node voltage) and branch currents using hand calculations. (Note, you may make reasonable approximations which simplifies things greatly).
 - b) Determine the small-signal AC parameters A_d ($=A_{do}$, since there is no R_L), R_{id} and R_{od} using hand calculations. (Note, there is no common mode to worry about since this is the active-load configuration. So you don't need to calculate A_{cm} ($=A_{cmo}$), R_{icm} and R_{ocm}).
 - c) In PSPICE, use Transfer Function Analysis with Bias Points Details turned on to verify your DC and AC hand-calculated values above. Remember to edit the BJT transistor models properly by setting BF and VAF. (Note that you cannot set V_{BE-on} in PSPICE). Remember to look at your xxx.out file for your answers. As usual, please turn in printouts of your *properly annotated* PSPICE schematic and *properly edit'ed and annotated* xxx.out file.

2. Repeat Problem 1 for the active-loaded MOS Differential Amplifier shown on reverse page. Assume the MOSFET's are matched and have the following model parameters: $V_{tn}=1V$, $K_n=250\mu A/V^2$, $\lambda_n=.02$, $V_{tp}=-1.5V$, $K_p=200\mu A/V^2$, $\lambda_p=.05$. In PSPICE, use Mbreakn3 and Mbreakp3 and edit their models properly by setting LAMBDA and VTO and, specifically, KP=500U for the nFET and KP=400U for the pFET.

