

# EE352 HW2 SOLUTIONS

- 1.) a.) DC node voltages and branch currents hand calcul  
 (See schematic below; hand calculated values are labeled and circled)
- b.) AC Hand Analysis:

$$g_{m1} = g_{m2} = \frac{I_C}{V_T} \approx 2 \text{ mA/V}^2$$


$$r_{o2} = \frac{V_{A1}}{I_2} = \frac{80}{50 \mu\text{A}} = 1.6 \text{ M}\Omega$$

$$r_{o4} = \frac{V_{A2}}{I_2} = \frac{130}{50 \mu\text{A}} = 2.6 \text{ M}\Omega$$

$$A_d = \frac{v_{o2}}{v_{in}} = g_{m1} (r_{o2} \parallel r_{o4}) = 1981 \text{ V/V}$$

$$R_{in} = 2r_{\pi} = 2 \frac{\beta_n}{g_m} = 150 \text{ K}\Omega$$
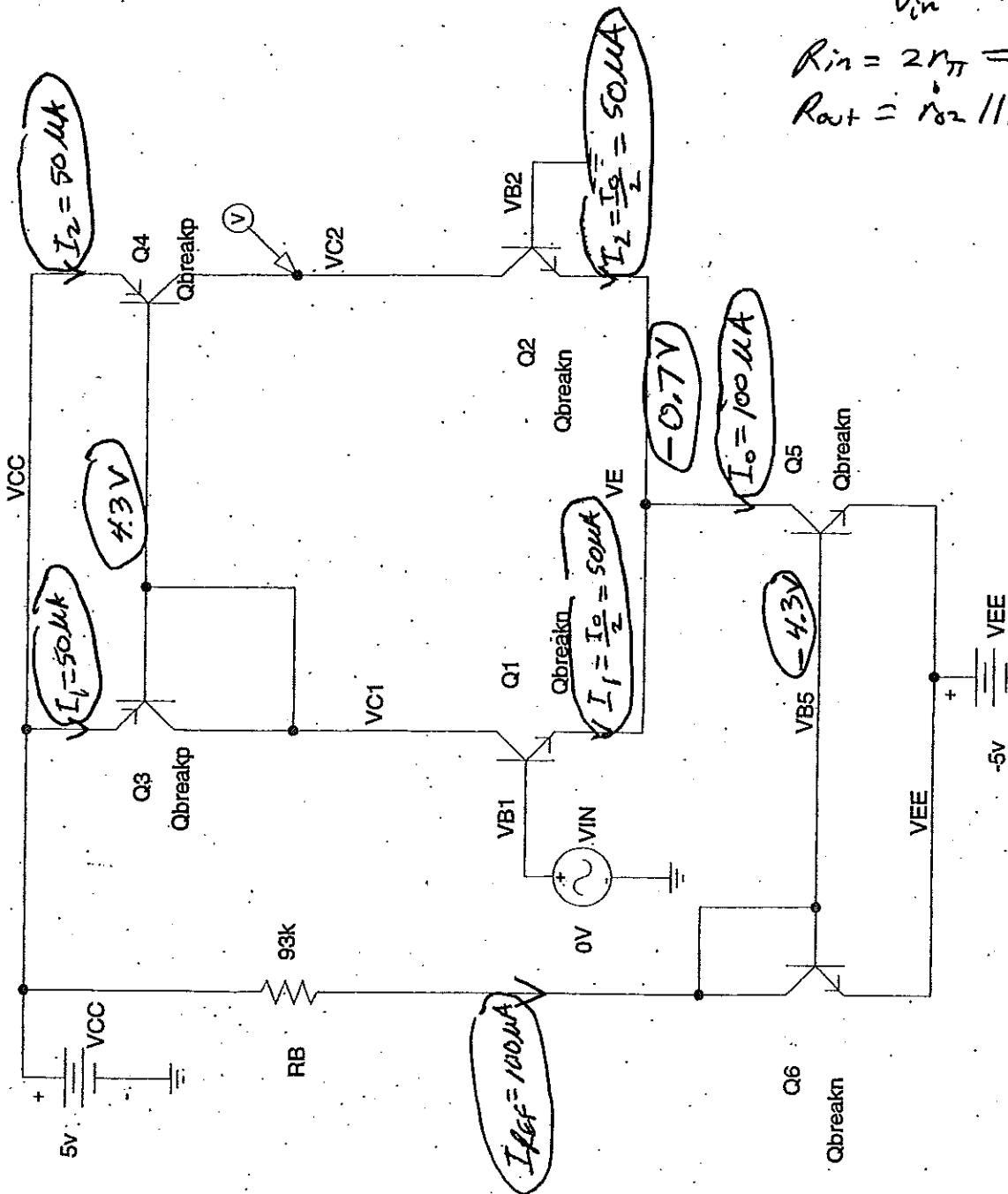
$$R_{out} = r_{o2} \parallel r_{o4} = 990 \text{ K}\Omega$$



DC node voltage and branch currents shown as circled.  
 hand-calculated

\*\*\*\* 01/30/102 10:07:45 \*\*\*\*\* PSpice 6.2 (April 1995) \*\*\*\*\* ID# 83989 \*\*\*\*

\* /usr1.c/oster/pspice/ee352/spring98/hw2/hw2a.sch

\*\*\*\* CIRCUIT DESCRIPTION

\*\*\*\*\*

\* Schematics Version 6.2 - April 1995

\* Wed Jan 30 10:07:40 2002

\*\* Analysis setup \*\*

.DC LIN V\_VIN -.1 .1 .001

.TF V([VC2]) V\_VIN

.OP

.LIB hw2a.lib

\* From [SCHEMATICS NETLIST] section of msim.ini:

.lib nom.lib

.INC "hw2a.net"

\*\*\*\* INCLUDING hw2a.net \*\*\*\*

\* Schematics Netlist \*

```

Q_Q1      VC1 VB1 VE Qbreakn
Q_Q2      VC2 0 VE Qbreakn
Q_Q3      VC1 VC1 VCC Qbreakp
Q_Q4      VC2 VC1 VCC Qbreakp
V_VCC     VCC 0 5v
V_VEE     VEE 0 -5v
V_VIN     VB1 0 DC 0V AC 0V
Q_Q5      VE VB5 VEE Qbreakn
Q_Q6      VB5 VB5 VEE Qbreakn
R_RB      VB5 VCC 93k
.probe
.END

```

1. out file

\*\*\*\* BJT MODEL PARAMETERS

\*\*\*\*\*

	Qbreakp PNP	Qbreakn NPN
IS	100.000000E-18	100.000000E-18
BF	100	150
NF	1	1
VAF	80	130
BR	1	1
NR	1	1

\*\*\*\* SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 27.000 DEG C

\*\*\*\*\*

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
( VE)	-0.6961	( VB1)	0.0000	( VB5)	-4.2857	( VC1)	4.3035
( VC2)	3.3083	( VCC)	5.0000	( VEE)	-5.0000		

VOLTAGE SOURCE CURRENTS

NAME	CURRENT
V_VCC	-2.004E-04
V_VEE	2.011E-04
V_VIN	-3.258E-07

TOTAL POWER DISSIPATION 2.01E-03 WATTS

\*\*\*\* OPERATING POINT INFORMATION TEMPERATURE = 27.000 DEG C

\*\*\*\*\*

\*\*\*\* BIPOLAR JUNCTION TRANSISTORS

NAME	Q_Q1	Q_Q2	Q_Q3	Q_Q4	Q_Q5
MODEL	Qbreakn	Qbreakn	Qbreakp	Qbreakp	Qbreakn
IB	3.26E-07	3.26E-07	-4.95E-07	-4.95E-07	6.57E-07
IC	5.05E-05	5.01E-05	-4.95E-05	-5.01E-05	1.01E-04
VBE	6.96E-01	6.96E-01	-6.96E-01	-6.96E-01	7.14E-01
VBC	-4.30E+00	-3.31E+00	0.00E+00	9.95E-01	-3.59E+00
VCE	5.00E+00	4.00E+00	-6.96E-01	-1.69E+00	4.30E+00
BETADC	1.55E+02	1.54E+02	1.00E+02	1.01E+02	1.54E+02

GM	1.95E-03	1.94E-03	1.91E-03	1.94E-03	3.91E-03
RPI	7.94E+04	7.94E+04	5.23E+04	5.23E+04	3.94E+04
RX	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
RO	2.66E+06	2.66E+06	1.62E+06	1.62E+06	1.32E+06
CBE	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CBC	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CBX	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CJS	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
BETAAC	1.55E+02	1.54E+02	1.00E+02	1.01E+02	1.54E+02
FT	3.11E+16	3.08E+16	3.04E+16	3.08E+16	6.23E+16

NAME	Q_Q6
MODEL	Qbreakn
IB	6.57E-07
IC	9.85E-05
VBE	7.14E-01
VBC	0.00E+00
VCE	7.14E-01
BETADC	1.50E+02
GM	3.81E-03
RPI	3.94E+04
RX	0.00E+00
RO	1.32E+06
CBE	0.00E+00
CBC	0.00E+00
CBX	0.00E+00
CJS	0.00E+00
BETAAC	1.50E+02
FT	6.06E+16

\*\*\*\*

SMALL-SIGNAL CHARACTERISTICS

V(VC2)/V\_VIN = 1.947E+03  
 INPUT RESISTANCE AT V\_VIN = 2.549E+05  
 OUTPUT RESISTANCE AT V(VC2) = 1.005E+06

JOB CONCLUDED  
 TOTAL JOB TIME

1.55

(2) a.) DC node voltages and branch currents hand calculation  
 (see schematic below; hand calculated DC values are labeled and circled).

$$I_1 = 100 \mu A = K_n (V_{GS} - V_{thn})^2 = 250 \mu A/V^2 [(0 - v_s) - 1]^2 \Rightarrow v_s = -1.63V$$

$$I_2 = 100 \mu A = K_p (V_{GS} - V_{thp})^2 = 200 \mu A/V^2 [(V_{DD} - v_{D1}) - 1.5]^2 \Rightarrow v_{D1} = 2.74V$$

b.) AC Hand Analysis:


$$g_{m1} = \sqrt{4K_n I_1} = 0.316 \text{ mA/V}^2$$

$$r_{o2} = \frac{1}{\lambda_2 I_2} = 500 \text{ K}\Omega; r_{o4} = \frac{1}{\lambda_4 I_2} = 260 \text{ K}\Omega$$

$$A_d = g_{m1} (r_{o2} || r_{o4}) = 45.1 \text{ V/V}$$

$$R_{in} = \infty$$

$$R_{out} = r_{o2} || r_{o4} = 143 \text{ K}\Omega$$

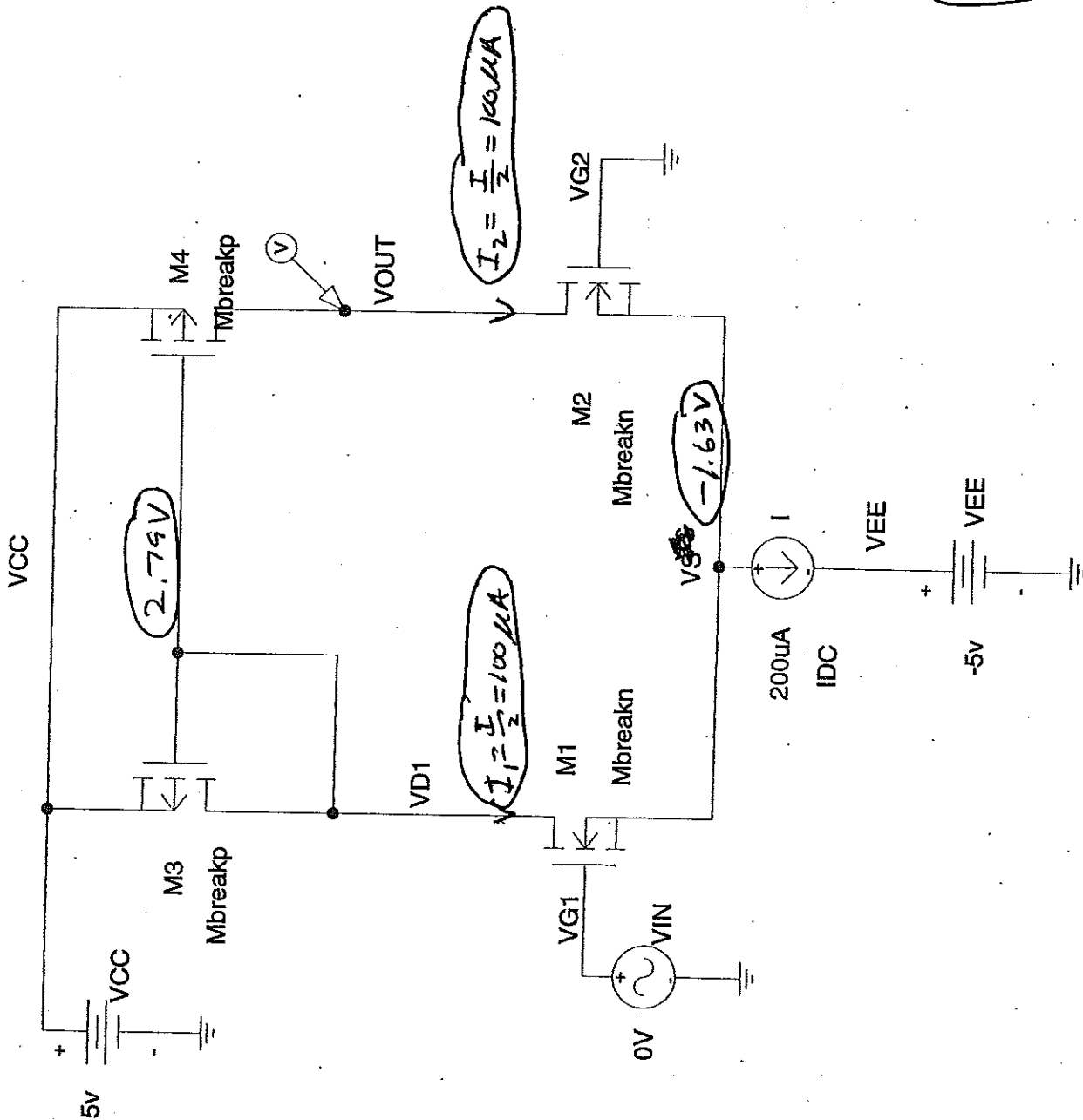

DC hand-calculated node voltages and branch currents shown above as circled

\*\*\*\* . CIRCUIT DESCRIPTION

\*\*\*\*\*

\* Schematics Version 6.2 - April 1995

\* Fri Feb 1 14:57:12 2002

\*\* Analysis setup \*\*

.DC LIN V\_VIN -.1 .1 .001

.TF V([VOUT]) V\_VIN

.OP

.LIB hw2b.lib

\* From [SCHEMATICS NETLIST] section of msim.ini:

.lib nom.lib

.INC "hw2b.net"

\*\*\*\* INCLUDING hw2b.net \*\*\*\*

\* Schematics Netlist \*

```

V_VCC      VCC 0 5v
V_VEE      VEE 0 -5v
V_VIN      VG1 0 DC 0V AC 0V
M_M1       VD1 VG1 VS VS Mbreakn
M_M2       VOUT 0 VS VS Mbreakn
M_M4       VOUT VD1 VCC VCC Mbreakp
M_M3       VD1 VD1 VCC VCC Mbreakp
I_I        VS VEE DC 200uA
.probe
.END

```

2.

out file

\*\*\*\* MOSFET MODEL PARAMETERS

\*\*\*\*\*

	Mbreakn	Mbreakp
	NMOS	PMOS
LEVEL	1	1
L	100.000000E-06	100.000000E-06
W	100.000000E-06	100.000000E-06
VTO	1	-1.5
KP	500.000000E-06	400.000000E-06
GAMMA	0	0
PHI	.6	.6
LAMBDA	.02	.05
IS	10.000000E-15	10.000000E-15
PBSW	.8	.8

\*\*\*\* SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 27.000 DEG C

\*\*\*\*\*

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
( VS)	-1.6061	( VCC)	5.0000	( VD1)	2.8284	( VEE)	-5.0000
( VG1)	0.0000	( VOUT)	2.8284				

VOLTAGE SOURCE CURRENTS

NAME	CURRENT
V_VCC	-2.000E-04
V_VEE	2.000E-04
V_VIN	0.000E+00

TOTAL POWER DISSIPATION 2.00E-03 WATTS

\*\*\*\* OPERATING POINT INFORMATION TEMPERATURE = 27.000 DEG C

\*\*\*\*\*

\*\*\*\* MOSFETS

NAME	M_M1	M_M2	M_M4	M_M3
MODEL	Mbreakp	Mbreakn	Mbreakp	Mbreakp
ID	1.00E-04	1.00E-04	-1.00E-04	-1.00E-04
VGS	1.61E+00	1.61E+00	-2.17E+00	-2.17E+00
VDS	4.43E+00	4.43E+00	-2.17E+00	-2.17E+00
VBS	0.00E+00	0.00E+00	0.00E+00	0.00E+00
VTH	1.00E+00	1.00E+00	-1.50E+00	-1.50E+00

VDSAT	6.06E-01	6.06E-01	-6.72E-01	-6.72E-01
GM	3.30E-04	3.30E-04	2.98E-04	2.98E-04
GDS	1.84E-06	1.84E-06	4.51E-06	4.51E-06
GMB	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CBD	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CBS	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CGSOV	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CGDOV	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CGBOV	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CGS	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CGD	0.00E+00	0.00E+00	0.00E+00	0.00E+00
CGB	0.00E+00	0.00E+00	0.00E+00	0.00E+00

\*\*\*\*

SMALL-SIGNAL CHARACTERISTICS

V(VOUT)/V\_VIN = 5.160E+01  
 INPUT RESISTANCE AT V\_VIN = 1.000E+20  
 OUTPUT RESISTANCE AT V(VOUT) = 1.580E+05

JOB CONCLUDED  
 TOTAL JOB TIME

1.57