

EE 352 HW 3 Solutions



File Edit Debug Desktop Window Help

New to MATLAB? Watch this video, see Demos, or read Getting Started.

```
>> s=tf('s')
```

```
Transfer function:
```

```
s
```

```
>> T=(1e4*(1+s/1e5))/((1+s/1e3)*(1+s/1e4))
```

```
Transfer function:
```

```
0.1 s + 10000
```

```
-----  
1e-007 s^2 + 0.0011 s + 1
```

```
>> bode(T)
```

```
>> [mag,phase]=bode(T,1e6)
```


```
mag =
```

```
1.0049
```

```
phase =
```

```
-95.0604
```

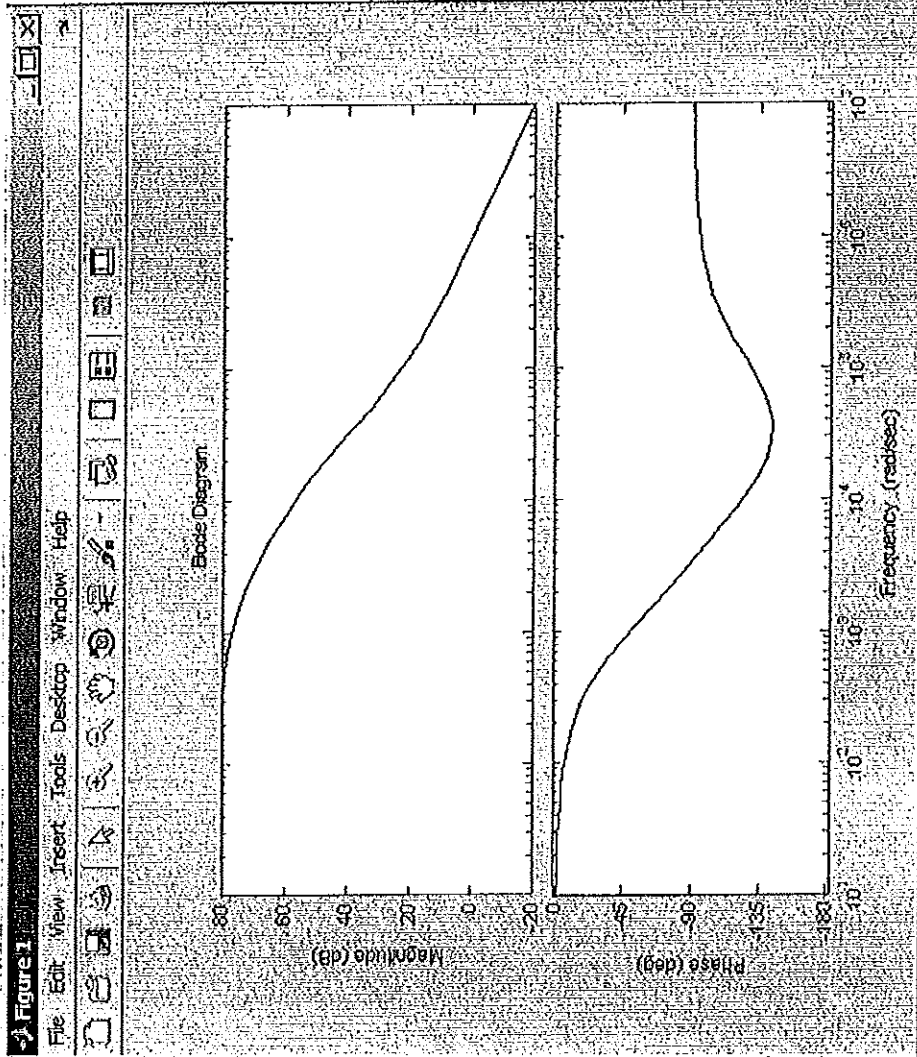
```
>>  
>>  
>>  
>>  
>>  
>>  
>>  
>>  
>>  
>>
```



Start | [Icons] | Shakespeare in Love | Th... | Spring 12

A-4 MATLAB

12:51 PM

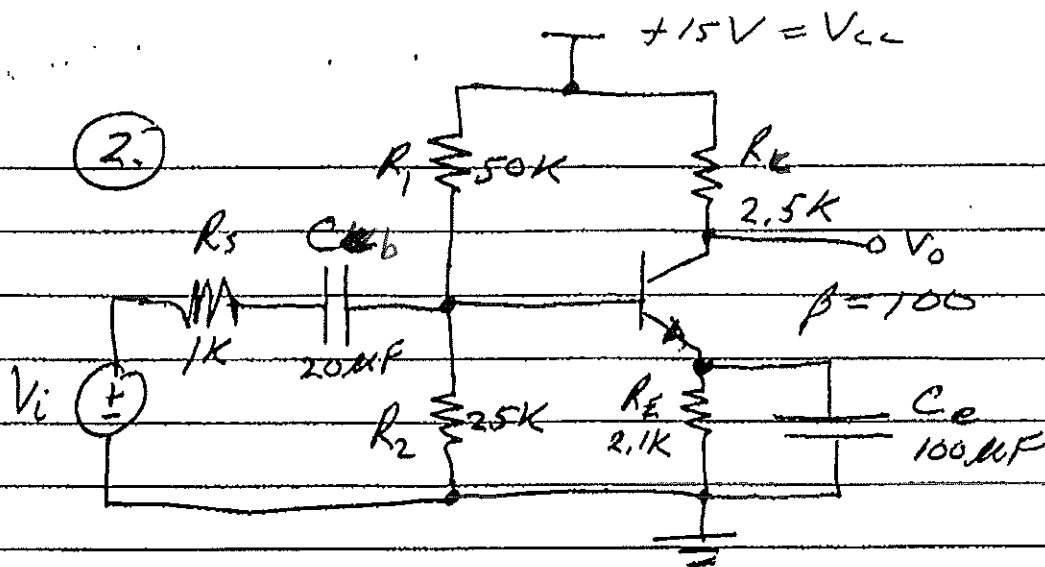

a) DC Analysis :

$$I_E = \frac{V_{BB} - V_{BE(on)}}{R_E + \frac{R_B}{1+\beta}} = \frac{5V - 0.7V}{2.1K + \frac{16.7K}{101}} = 1.9mA$$

$$I_C = \alpha I_E = \frac{100}{101} I_E = 1.88mA$$

$$I_B = I_C / \beta = 18.8\mu A$$

$$V_E = I_E R_E = 3.99V$$

$$V_B = V_E + V_{BE(on)} = 4.69V$$


$$V_C = V_{CC} - I_C R_C = 15 - (1.88mA) 2.5K = 10.3V$$

$$I_{R1} = \frac{V_{CC} - V_B}{R_1} = 0.21mA$$

$$I_{R2} = \frac{V_B}{R_2} = 0.19mA$$

Yes; Bias stable to Temp \checkmark
 due to $V_{BB} \gg V_{BE}$; $5V \gg 0.7V$
 and to β dec to
 $R_E \gg \frac{R_B}{1+\beta}$; $2.1K \gg \frac{16.7K}{101}$ \checkmark

b) AC SS Midband Analysis:

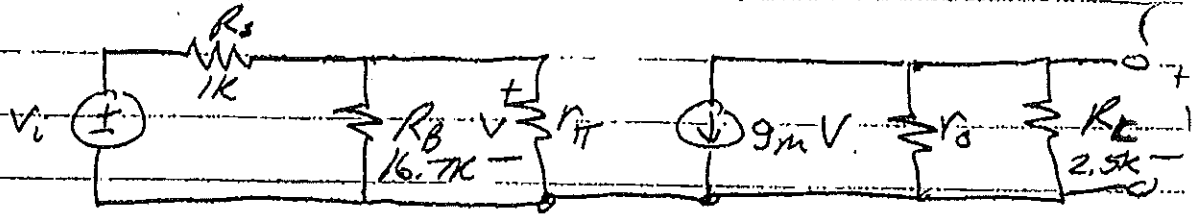


$$g_m = \frac{I_c}{V_T} = 0.075 \text{ A/V}; r_{\pi} = \frac{\beta}{g_m} = 1330 \Omega;$$

$$r_o = 1/h_{oe} = 66.7 \text{ K}\Omega$$

$$A_m = \left| \frac{V_o}{V_i} \right| = \frac{g_m r_{\pi} \parallel R_B (r_o \parallel R_L)}{r_{\pi} \parallel R_B + R_S} = 99.7$$

$$R_i = R_B \parallel r_{\pi} = 1.23 \text{ K}\Omega; R_o = r_o \parallel R_L = 2.41 \text{ K}\Omega$$

AC SS Full Freq Response Analysis:

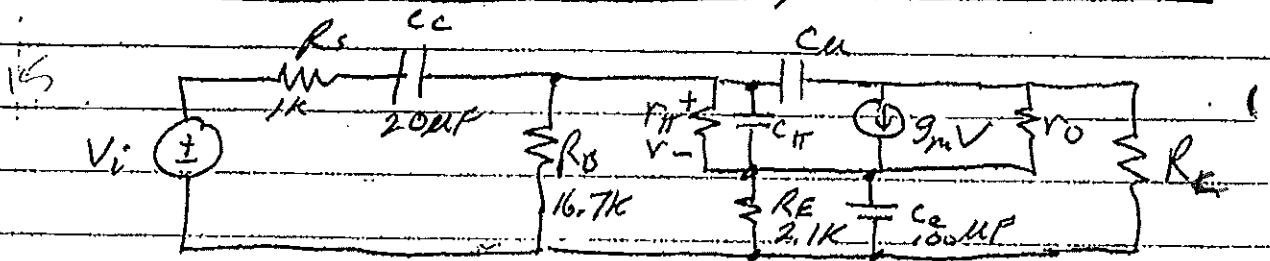

$$C_{CU} = C_{Cob} = 4 \text{ pF}$$

C_{π} - recipe

$$C_{\pi} / 10 \mu\text{A} = \frac{g_m / 10 \mu\text{A}}{2\pi \cdot 56 \text{ kHz}} - C_{CU} = C_{b1} / 10 \mu\text{A} + C_{ibe}$$

$$C_{\pi} / 10 \mu\text{A} = \frac{4 \text{ V/A}}{2\pi (300 \text{ kHz})} - 4 \text{ pF} = 208 \text{ pF}$$

$$\therefore C_{b1} / 10 \mu\text{A} = 208 \text{ pF} - 8 \text{ pF} = 200 \text{ pF}$$

$$\text{Scale } C_b: C_{b1} / 1.88 \text{ mA} = \frac{1.88}{10} (200 \text{ pF}) = 37.6 \text{ pF}$$

$$\therefore C_{\pi} / 1.88 \text{ mA} = C_{\pi} = 37.6 \text{ pF} + 8 \text{ pF} = 45.6 \text{ pF}$$

Calculate ω_L using GCTC'S:

$$\omega_L \leq \sum \frac{1}{\omega_{p_i}} = \frac{1}{R_{s_i} C_{s_i}} + \frac{1}{R_{e_i} C_{e_i}}$$

$$\omega_L \leq \frac{1}{(R_s + r_{\pi} || R_B) C_B} + \frac{1}{R_E (r_{\pi} + R_s || R_B) C_E}$$


$$\omega_L \approx 2\pi (75 \text{ Hz}) \quad 971$$

$$\omega_H \approx \frac{1}{\sum \tau_{p_i}} = \frac{1}{R_{e_H} C_{e_H} + R_{c_{\pi}} C_{\pi}}$$

$$\omega_H \approx (r_{\pi} || R_B || R_s) C_{\pi} + [R_o || R_L + R_{\pi} || R_B || R_s (1 + g_m R_o || R_L)]$$

$$\omega_H \approx 2\pi (365 \text{ kHz})$$

Bode Plot:

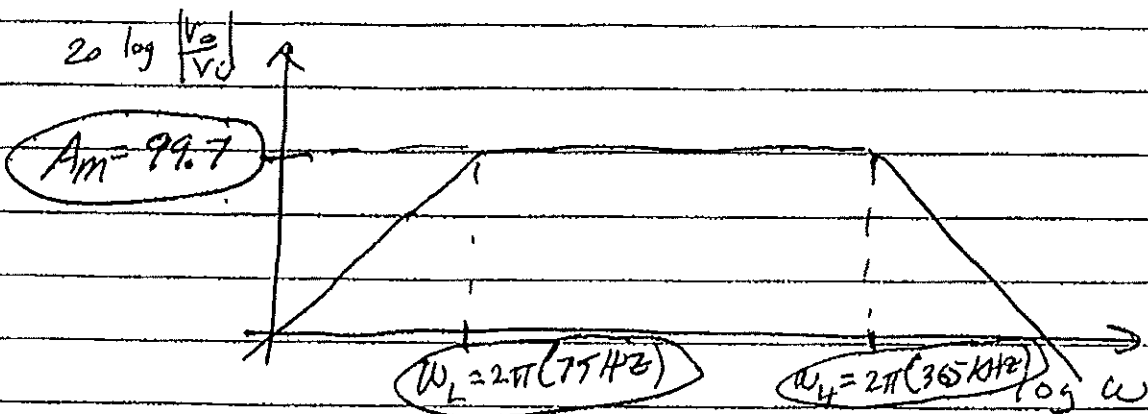

$$c) f_c = f_t / 1.58 \text{ mA} = \frac{9 \text{ mV} \cdot 58 \text{ mA}}{2\pi (C_{\pi} / 1.58 \text{ mA} + C_{e_H})} = 241 \text{ MHz}$$

$$2) R_{in} = R_B || R_s = 2.2 \text{ k}\Omega$$

$$R_{out} = R_s || R_L = 2.4 \text{ k}\Omega$$

$$1) \frac{V_A}{f_c} = \frac{1}{100} \Rightarrow V_A = 125 \text{ V}$$


2.


PSPICE DC

Verluste Schauen

(All against well with Head)

PSPICE
XXX. sch
Schematic

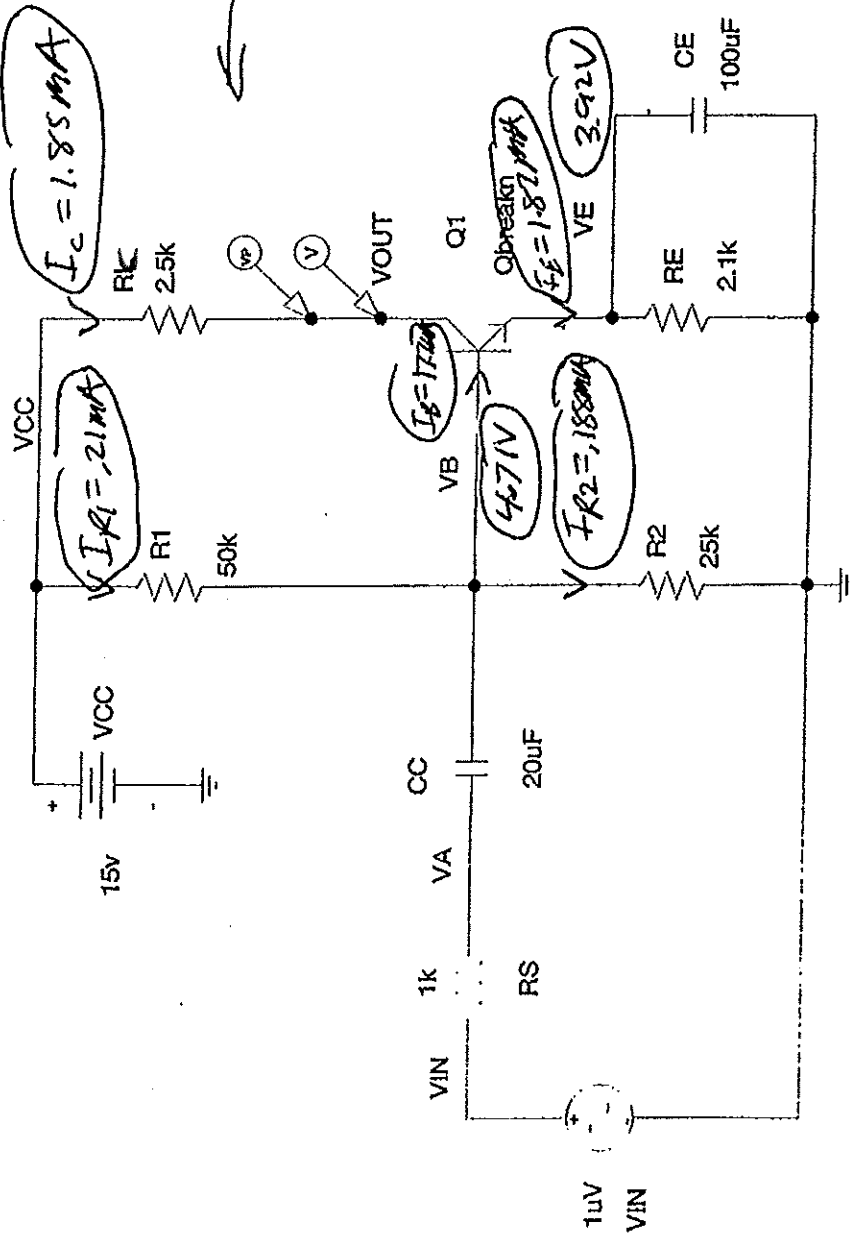

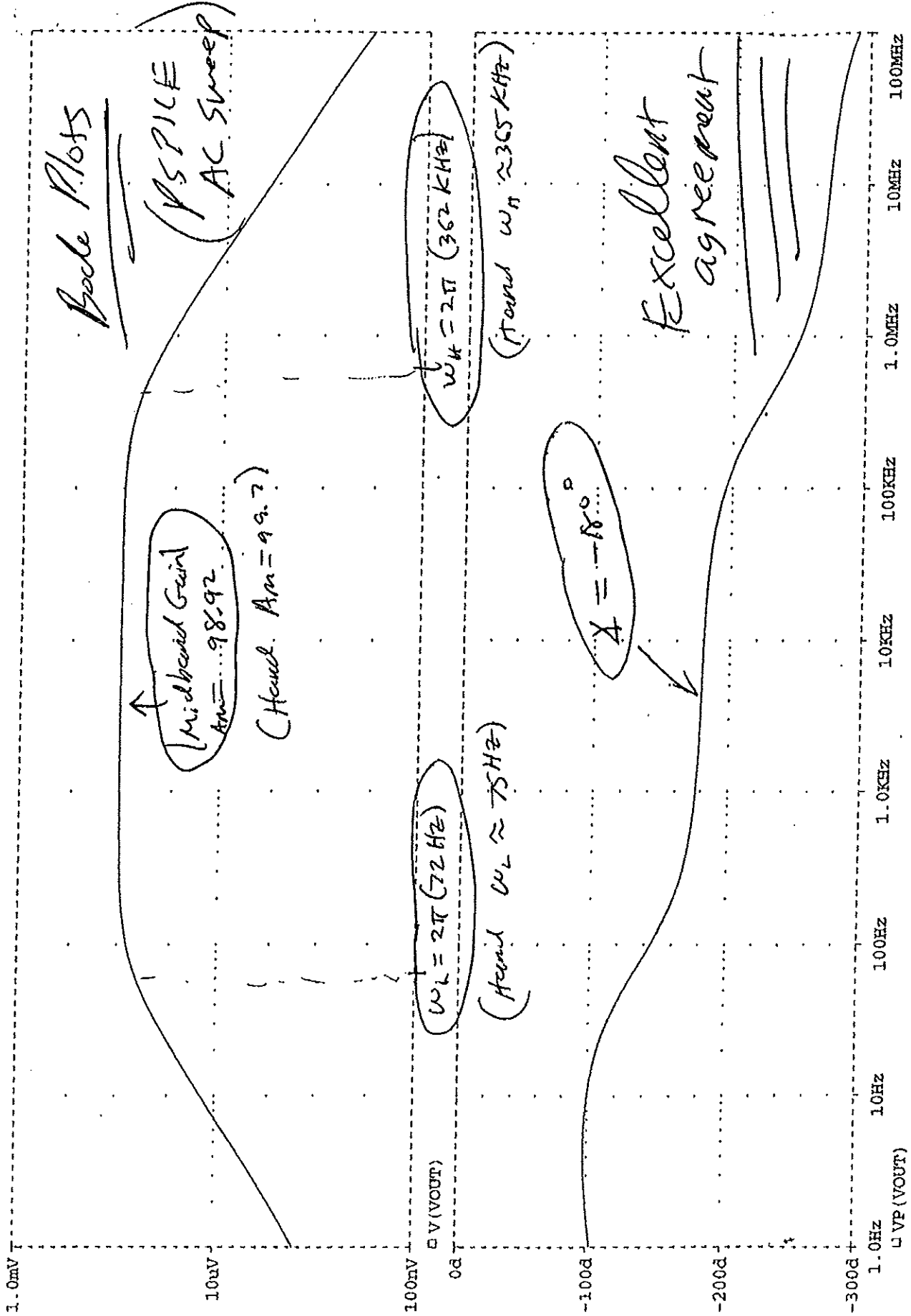

**** CIRCUIT DESCRIPTION

* Schematics Version 6.2 - April 1995

* Thu Feb 11 18:47:26 1999

** Analysis, setup **

.ac DEC 10 1 100MEG

.OP

```

Q_Q1      VOUT VB VE Qbreakn
R_RL      VOUT VCC 2.5k
R_RE      0 VE 2.1k
R_R2      0 VB 25k
R_R1      VB VCC 50k
R_RS      VA VIN 1k
C_CC      VA VB 20uF
C_CE      0 VE 100uF
V_VIN     VIN 0 DC 0V AC 1uV
V_VCC     VCC 0 15v
.probe
.END

```

*PSPICE
xxx.out
file*

**** BJT MODEL PARAMETERS

```

Qbreakn
NPN
BF 100
VAF 126
CJE 8.000000E-12
MJE 0
CJC 4.000000E-12
MJC 0
TF 500.000000E-12

```

} NPN Model parameters

**** SMALL SIGNAL BIAS SOLUTION

TEMPERATURE = 27.000 DEG C

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(VA)	0.0000	(VB)	4.7054	(VE)	3.9164	(VCC)	15.0000
(VIN)	0.0000	(VOUT)	10.3820				

TOTAL POWER DISSIPATION 3.08E-02 WATTS

All agree with Hand

**** BIPOLAR JUNCTION TRANSISTORS

```

NAME      Q_Q1
MODEL     Qbreakn
IB         1.77E-05
IC         1.85E-03
VBE        7.89E-01
VBC        -5.68E+00
VCE        6.47E+00
BETADC     1.05E+02
GM         7.14E-02
RPI        1.46E+03
RX         0.00E+00
RO         7.13E+04
CBE        4.37E-11
CBC        4.00E-12
CBX        0.00E+00
CJS        0.00E+00
BETAAC     1.04E+02
FT         2.38E+08

```

All Agree with Hand values