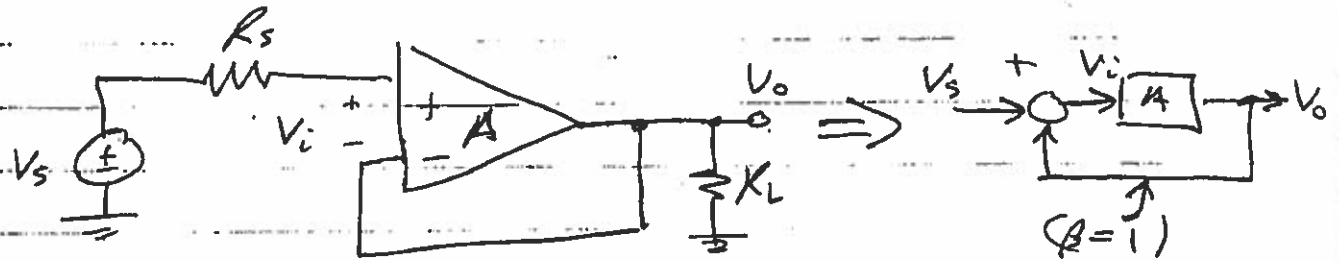


EE352 HW5 Solutions

11.3
 (11) Text ~~10.3~~



$$A_f = \frac{V_o}{V_s} = \frac{A}{1+A\beta} = \frac{A}{1+A}; \quad A\beta = A \Rightarrow \boxed{\beta = 1}$$

For $A = 1000$: $A_f = \frac{A}{1+A} = \frac{1000}{1001} = 0.999 \text{ V/V}$


Amt of Feedback = $1 + A\beta = 1001$
 $= 60 \text{ dB}$

For $V_s = 1 \text{ V}$:

$$V_o = 0.999 \text{ V}$$

$$V_i = \frac{V_o}{A} = \frac{0.999}{1000} = 0.999 \text{ mV}$$
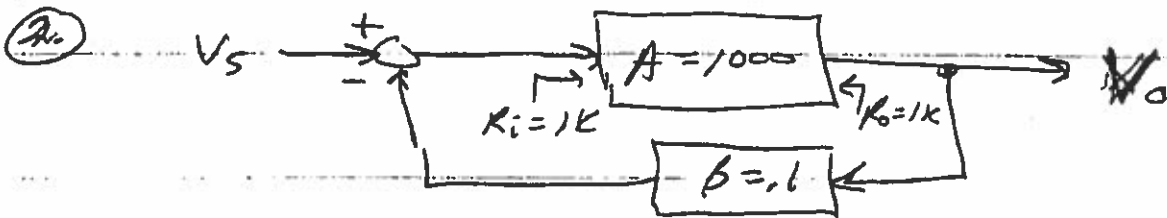
$$\frac{dA_f}{A_f} = \frac{1}{1+A\beta} \frac{dA}{A} = \frac{1}{1001} (-10\%) = -0.00999\%$$




$$A_f = \frac{V_o}{V_s} = \frac{A}{1+AB} = \frac{1000}{1+100} \approx 9.9\% \approx 10\%$$

$$R_{if} = R_i(1+AB) = 1K(1+100) = 101K\Omega$$

$$R_{of} = \frac{R_o}{1+AB} = \frac{1K}{1+100} = 9.9\Omega$$

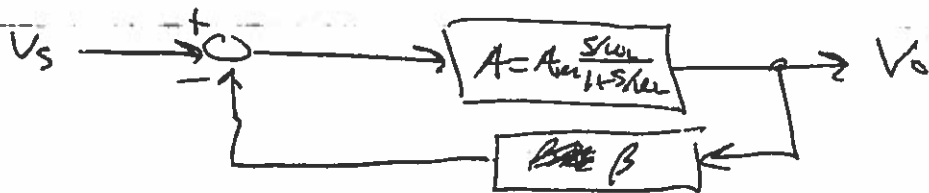3. Text 11.18

$$A = A_m \frac{s/\omega_L}{1+s/\omega_L} \quad (\text{Given})$$





$$A_f = \frac{V_o}{V_s} = \frac{A}{1+AB} = \frac{A_m \frac{s/\omega_L}{1+s/\omega_L}}{1 + \frac{A_m \beta s/\omega_L}{1+s/\omega_L}}$$

$$\therefore A_f = \left(\frac{A_m}{1+A_m\beta} \right) \frac{s(\omega_L/1+A_m\beta)}{1 + s(\omega_L/1+A_m\beta)}$$


$$\therefore A_m \rightarrow \frac{A_m}{1+A_m\beta}$$

$$\therefore \omega_L \rightarrow \frac{\omega_L}{1+A_m\beta}$$

5: Text \uparrow 11.24

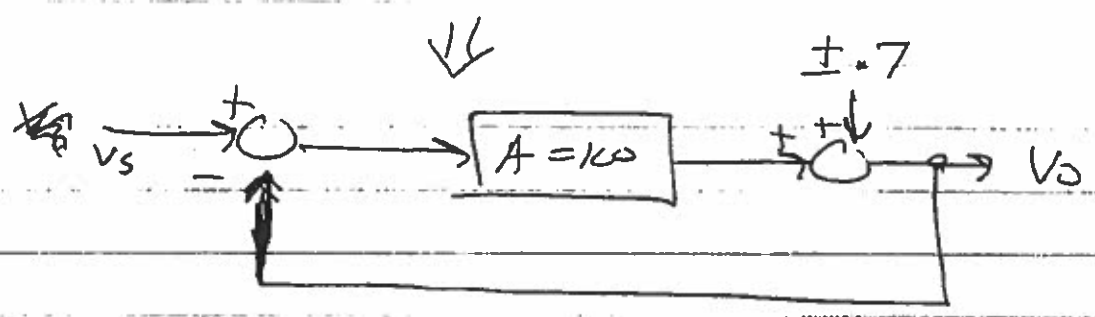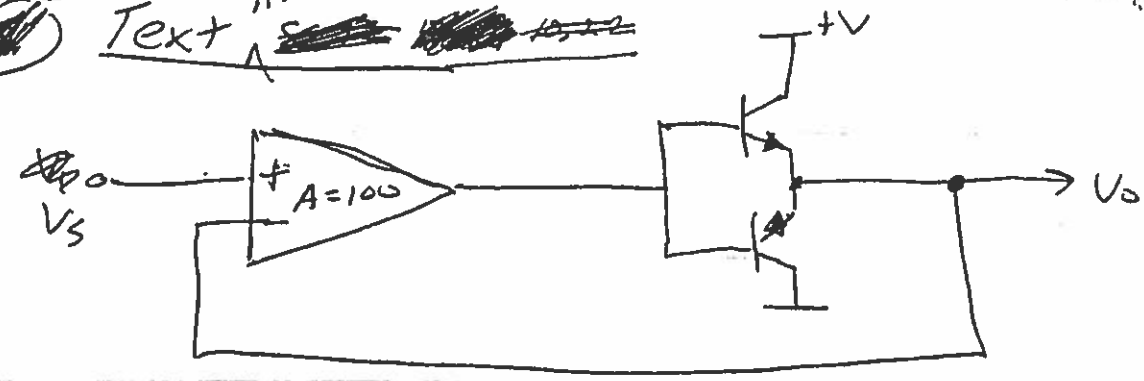
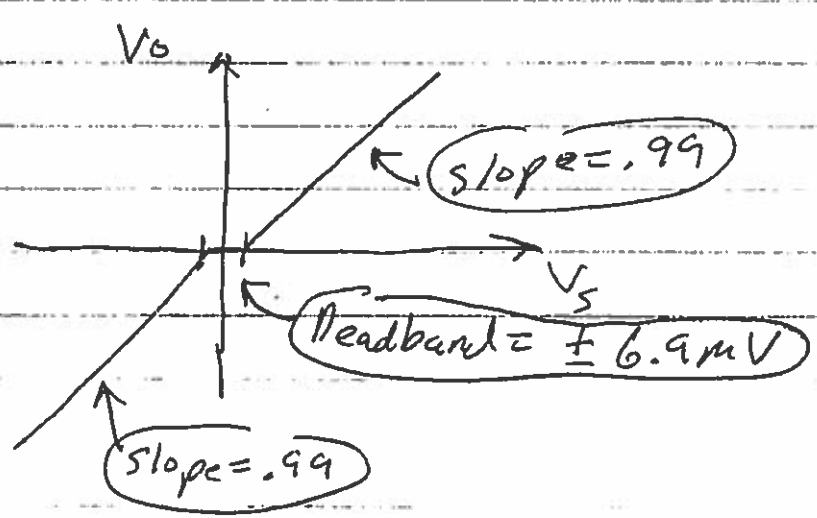
$$V_o = \frac{A}{1+A} V_s \pm \frac{0.7}{1+A} = .99 V_s \pm 6.9 \mu V$$



Note: Vast improvement from original DC Transfer Curve:

