

The University of Portland
Donald P. Shiley School of Engineering

EE352 Electronic Circuits II
HOMEWORK 8

Assigned: Wed, April 8, 2020
Due: Wed, April 22, 2020
Final Exam: Tues, Apr 28, 2020, 8am to 10am
(open-book, open-notes, calculator, three crib-sheets, Diff Amp sheet, Calculator sheet)

Problems:

- 1) Text 17.25. Use MATLAB to generate the Bode Plots and Step Response.
- 2) Text 17.26. Use MATLAB to generate the Bode Plots and Step Response.
- 3) Text 17.29. Use MATLAB to generate the Bode Plots and Step Response.
- 4) Consider the DC-to-DC Converter Charge Pump below. It is a “voltage quintupler”. First, analyze the circuit by hand. Assume the diodes are ideal. Hand in a table showing Φ_1 , Φ_2 , V_1 , V_2 , V_3 , V_4 , and V_5 (like we did in class). Then simulate the circuit in PSpICE. Use five Dbreak diodes and set their model parameters as follows: $I_S=1e-18$, $C_{JO}=.001pF$, and $R_S=0$. Hand in your Probe Output printout showing Φ_1 , Φ_2 , V_1 , V_2 , V_3 , V_4 , and V_5 . For Φ_1 , set $V_1=0$, $V_2=10V$, $TD=1mS$, $TR=0$, $TF=0$, $PW=1mS$, $PER=4mS$. For Φ_2 , set $V_1=0$, $V_2=10V$, $TD=3mS$, $TR=0$, $TF=0$, $PW=1mS$, $PER=4mS$. In the Analysis Setup menu, check Transient, and set Print Step=.01mS, Final Time=200mS.

