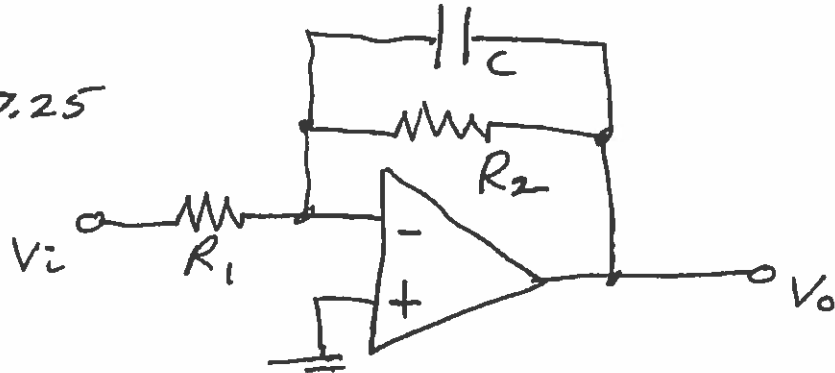


EE 352 HW 8 Solutions

1. Text 17.25



$$T(s) = \left(-\frac{R_2}{R_1}\right) \left[\frac{1}{1 + R_2 C s}\right]$$



$$R_{in} = 12K \Rightarrow R_1 = 12K$$

$$\left|-\frac{R_2}{R_1}\right| = 10 \Rightarrow R_2 = 120K$$


$$\omega_H = \frac{1}{R_2 C} = 2\pi (5KHz)$$

$$\Rightarrow C = 265PF$$

Matlab Bode Plots

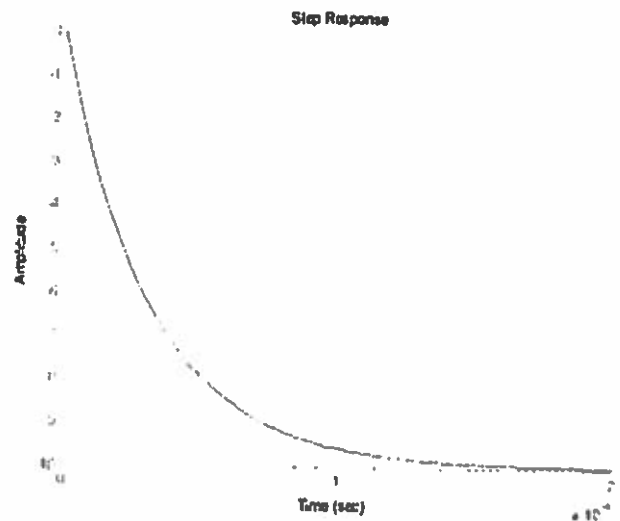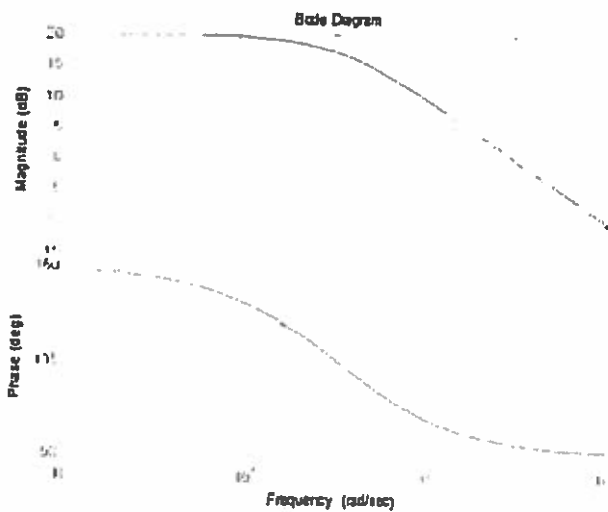

(2) Text 17.26

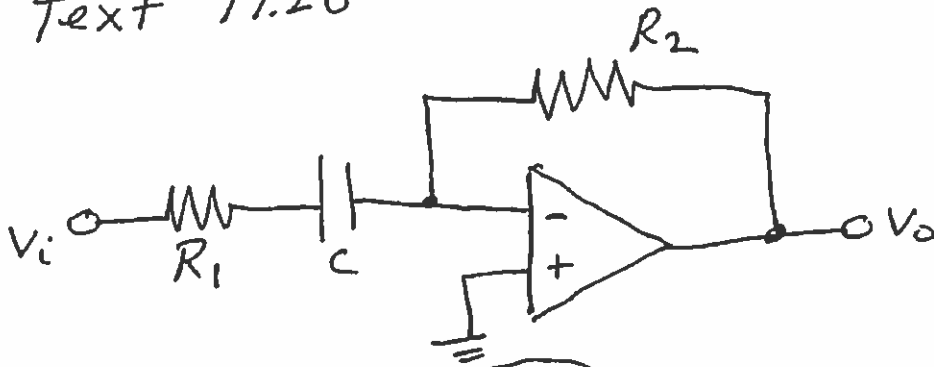

$$T(s) = \left(-\frac{R_2}{R_1}\right) \left[\frac{R_1 C s}{1 + R_1 C s}\right]$$



$$R_{in} = 120K \Rightarrow R_1 = 120K$$

$$\left|-\frac{R_2}{R_1}\right| = 1 \Rightarrow R_2 = 120K$$


$$\omega_L = \frac{1}{R_1 C} = 2\pi(200 \text{ Hz})$$

$$\Rightarrow C = 6.6 \text{ nF}$$

Matlab Plots

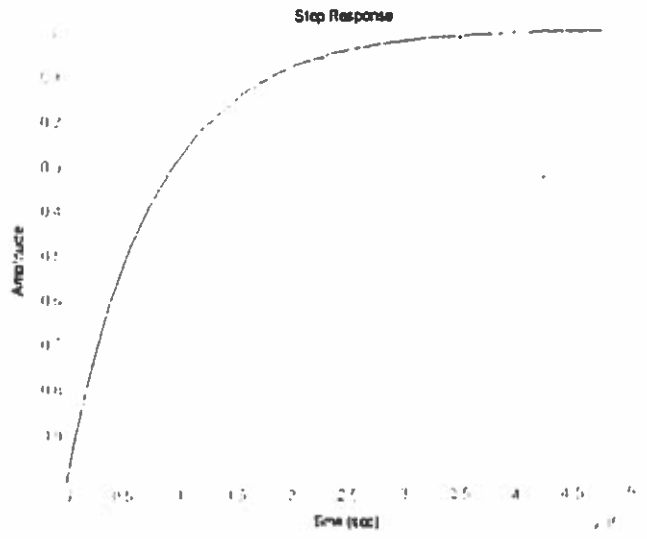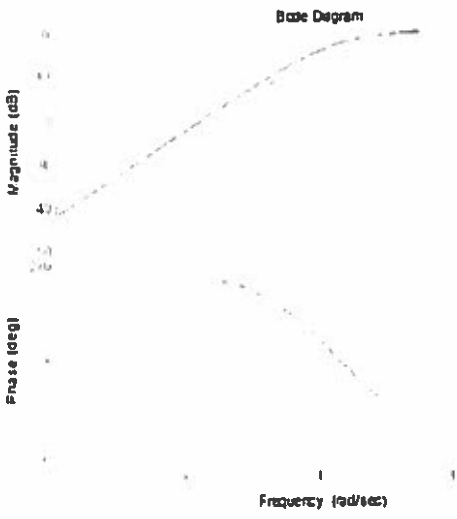

3. Text 17.29

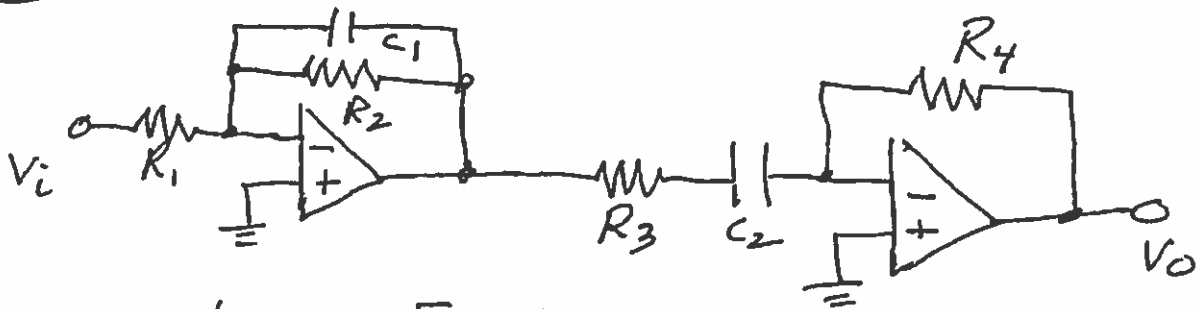

$$T(s) = \left(\frac{R_2 R_4}{R_1 R_3} \right) \left[\frac{R_3 C_2 s}{(1 + R_3 C_2 s)(1 + R_2 C_1 s)} \right] = A_m \frac{s/\omega_L}{(1 + s/\omega_L)(1 + s/\omega_H)}$$

$$A_m = \frac{R_2 R_4}{R_1 R_3} = 4; \omega_L = \frac{1}{R_3 C_2} = 2\pi(50\text{Hz}); \omega_H = \frac{1}{R_2 C_1} = 2\pi(50\text{kHz})$$


All R 's $\leq 100\text{k}$; $R_{in} = \text{Max} \Rightarrow R_1 = 100\text{k}$

Select $R_2 = R_4 = 100\text{k} \Rightarrow R_3 = 25\text{k}$

$\Rightarrow C_1 = 31.8\text{pF}$ $C_2 = 127\text{nF}$

(This is just one of an infinite # of valid solutions)


Matlab Bode Plots

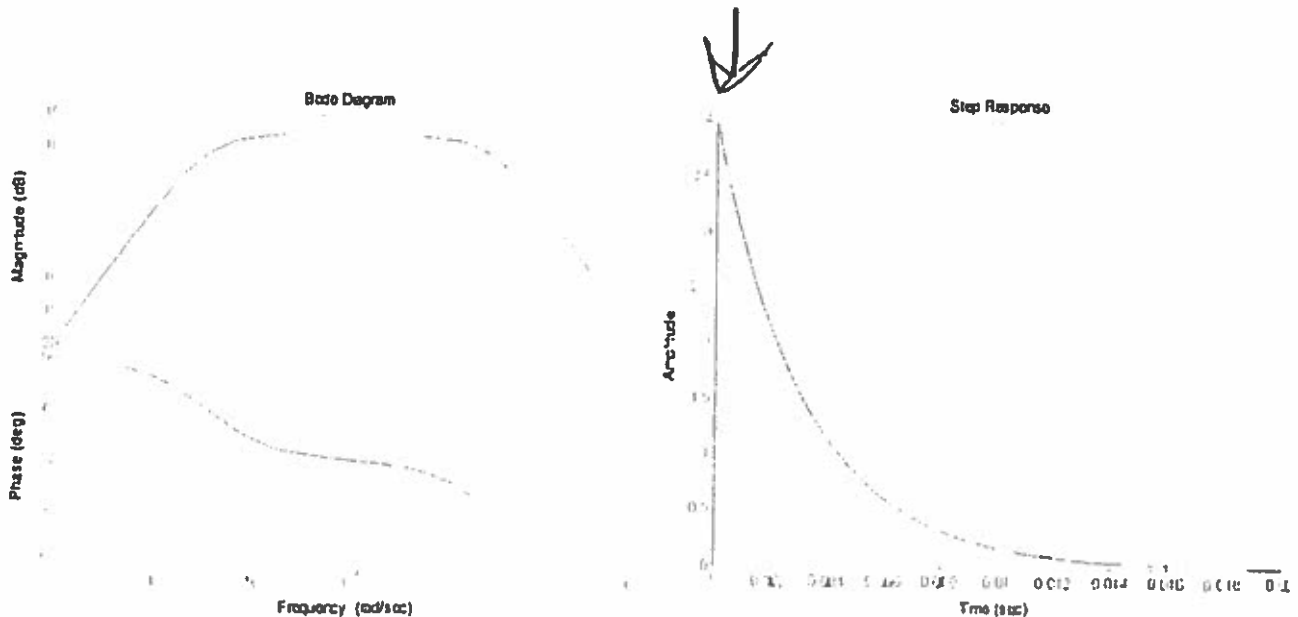

4.

~~Optional Bonus Problem (25 pts)~~

~~Voltage~~ Voltage quintupler

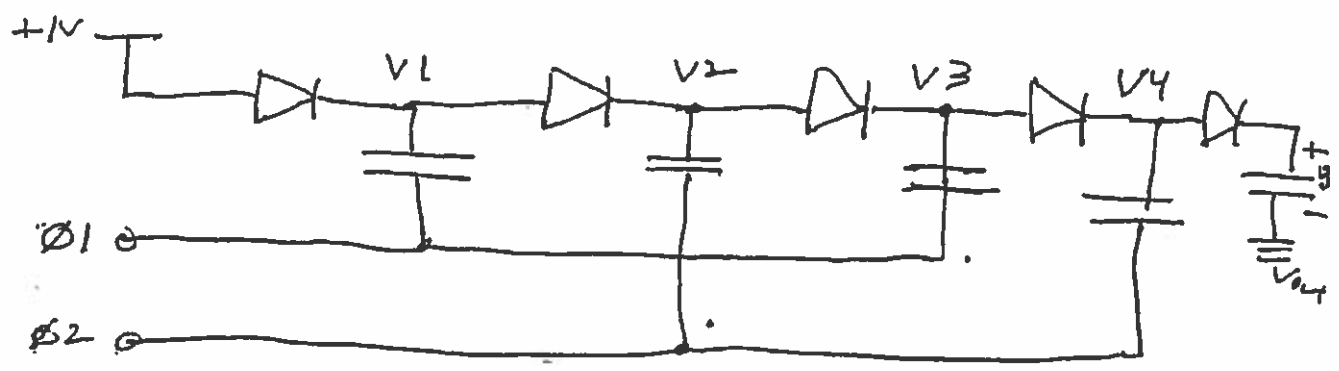


B1 0 1 0 0 0 1 0 0 0 1 0 0 0 1 0 0 0 1 0 0 0 1 0 0 0 1 0

B2 0 0 0 1 0 0 0 1 0 0 0 1 0 0 0 1 0 0 0 1 0 0 0 1 0 0 0


V1	1	2	1	1	2	1	1	1	2	1	1	1	2	1	1	1	2	1	1	2	1	1	1	2	1		
V2	1	2	1	2	1	2	2	3	2	2	2	3	2	2	2	3	2	2	2	3	2	2	2	3	2	2	
V3	1	2	1	2	2	3	2	3	3	4	3	3	3	4	3	3	3	4	3	3	3	4	3	3	3	4	3
V4	1	2	2	3	2	3	3	4	3	4	4	5	4	4	4	5	4	4	4	5	4	4	4	5	4	4	4
out	1	2	2	3	3	3	3	4	4	4	4	5	5	5	5	5	5	5	5	5	5	5	5	5	5	5	5

Vout → 5V

Quintupler

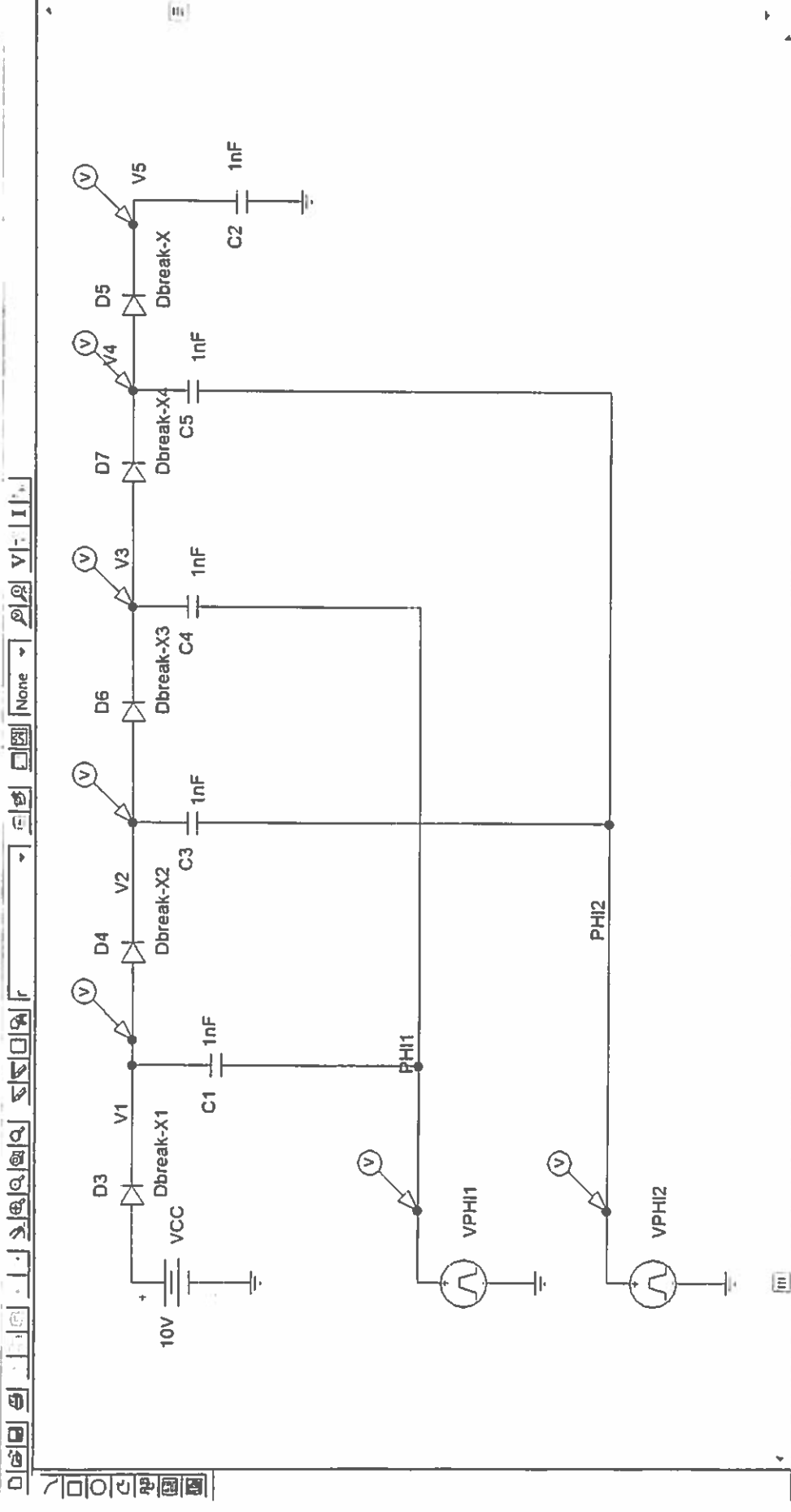

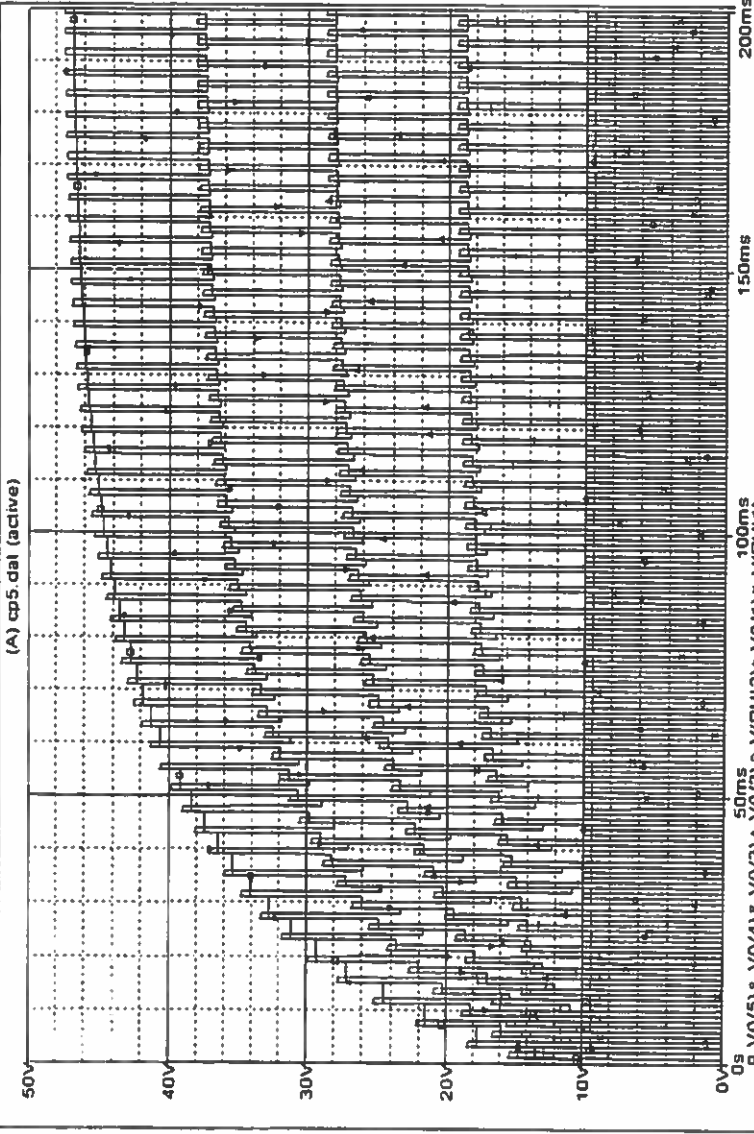Date/Time: run: 04/27/17 10:24:35
* U:\electrical_engineering\hoster\pspice\ee352\spring16\chargepump\cp5\cp5.sch Temperature: 27.0



0s 50ms 100ms 150ms 200ms
V(V5) * V(V4) * V(V3) * V(V2) * V(V1) * V(PH1)
Time
Date: April 27, 2017 Page 1

1009 10:25 AM 4/27/2017