


The University of Portland
Donald P. Shiley School of Engineering

EE352 Electronic Circuits II
Optional Extra Credit Homework

Assigned: Mon, April 13, 2020
Due: Mon, April 20, 2020, midnight as a pdf attachment
Final Exam: Tues, April 28, 2020, 8am to 10am
(open-book, open-notes, calculator, three crib-sheets, Diff Amp sheet, Calculator sheet)

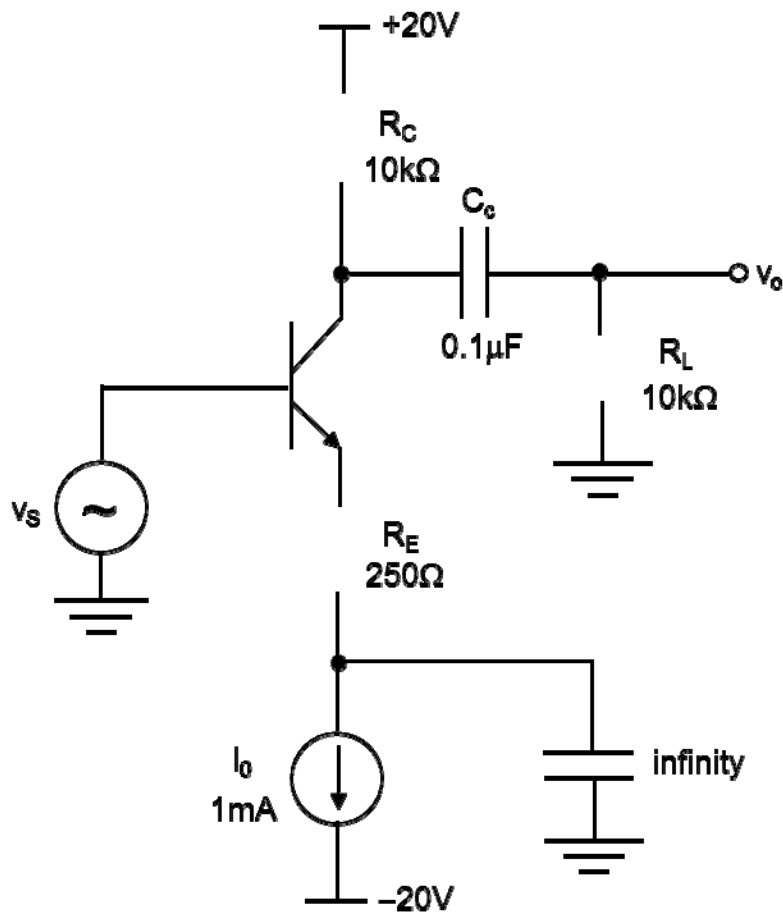Problem: (no partial credit; total points added to your homework 8 grade):

Consider the following BJT CE Amplifier with emitter-degeneracy. Assume $\beta=100$, $V_{BE-on}=0.7V$, $C_{\pi}=20pF$, $C_{\mu}=2pF$, $r_o=infinity$, and $V_T=25mV$. For simplicity, you may assume that $\tau_{C\pi}=R_{C\pi}C_{\pi}=0$ in part h below.



- a) **(5 points)** DC Analysis: Calculate I_C , V_E , and V_C . (**Note:** please make reasonable approximations when doing these calculations).
- b) **(5 points)** Neatly sketch the full AC SS model (including the Hybrid-Pi model, etc, as usual).
- c) **(5 points)** AC Midband Analysis: Calculate A_M .
- d) **(5 points)** Using your A_M expression from part c above, what does your A_M expression become as $\beta \rightarrow \infty$? (Isn't this a really neat result?)
- e) **(5 points)** AC Midband Analysis: Calculate R_{in} .
- f) **(5 points)** AC Midband Analysis: Calculate R_{out} (looking back into the circuit before R_L).
- g) **(5 points)** AC Low Frequency Analysis: Calculate ω_L using SCTC's.
- h) **(5 points)** AC High Frequency Analysis: Calculate ω_H using OCTC's. (Remember, for simplicity, you may assume that $\tau_{C\pi} = R_{C\pi}C_{\pi} = 0$).
- i) **(5 points)** Calculate the f_T of the BJT.
- j) **(50 points)** Simulate the circuit in PSPICE using AC Sweep Analysis. Set C_e to $100\mu F$. Use the following model parameters for your QBREAKN3: $BF=100$, $TF=500pS$, $CJC=2pF$, $CJE=0$, $MJC=0$, $MJE=0$. Hand in properly annotated PSPICE schematic, .out file, and AC Sweep output. In your PSPICE schematic, .out file or AC Sweep output graph, please highlight the following: I_C , V_E , V_C , A_M , f_L , f_H , g_m , r_{π} , r_o , C_{π} , C_{μ} and f_T , and compare to your hand calculations above.