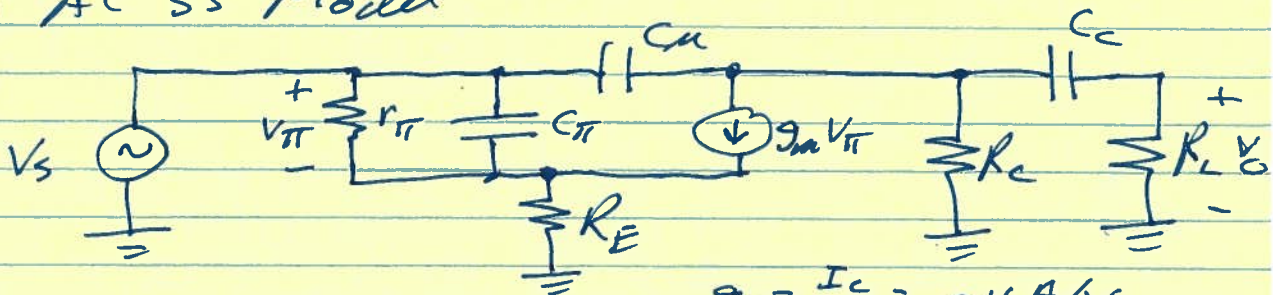


a.) $I_C = 1\text{mA}$ $V_E = -0.7\text{V}$ $V_C = 10\text{V}$

b.) AC SS Model



$$g_m = \frac{I_C}{V_T} = 0.04\text{A/V}$$

$$r_{\pi} = \frac{\beta}{g_m} = 2.5\text{K}\Omega$$

c.) $A_m = \frac{-\beta [R_L \parallel R_C]}{r_{\pi} + R_E (1 + \beta)} = -18\text{V/V}$

d.) $A_m \approx \frac{R_L \parallel R_C}{R_E} = -20\text{V/V}$ (for $\beta \rightarrow \infty$)


e.) $R_{in} = \frac{V_T}{I_T} = r_{\pi} + R_E (1 + \beta) = 27.75\text{K}\Omega$


f.) $R_{out} = R_C = 10\text{K}\Omega$

g.) $\omega_L = \frac{1}{\tau_{C_C}} = \frac{1}{(R_C \parallel R_L) C_C} = 500\text{rad/sec}$

h.) $\omega_H = \frac{1}{\tau_{C_{\pi}}} = \frac{1}{(R_C \parallel R_L) C_{\pi}} = 10^8\text{rad/sec}$

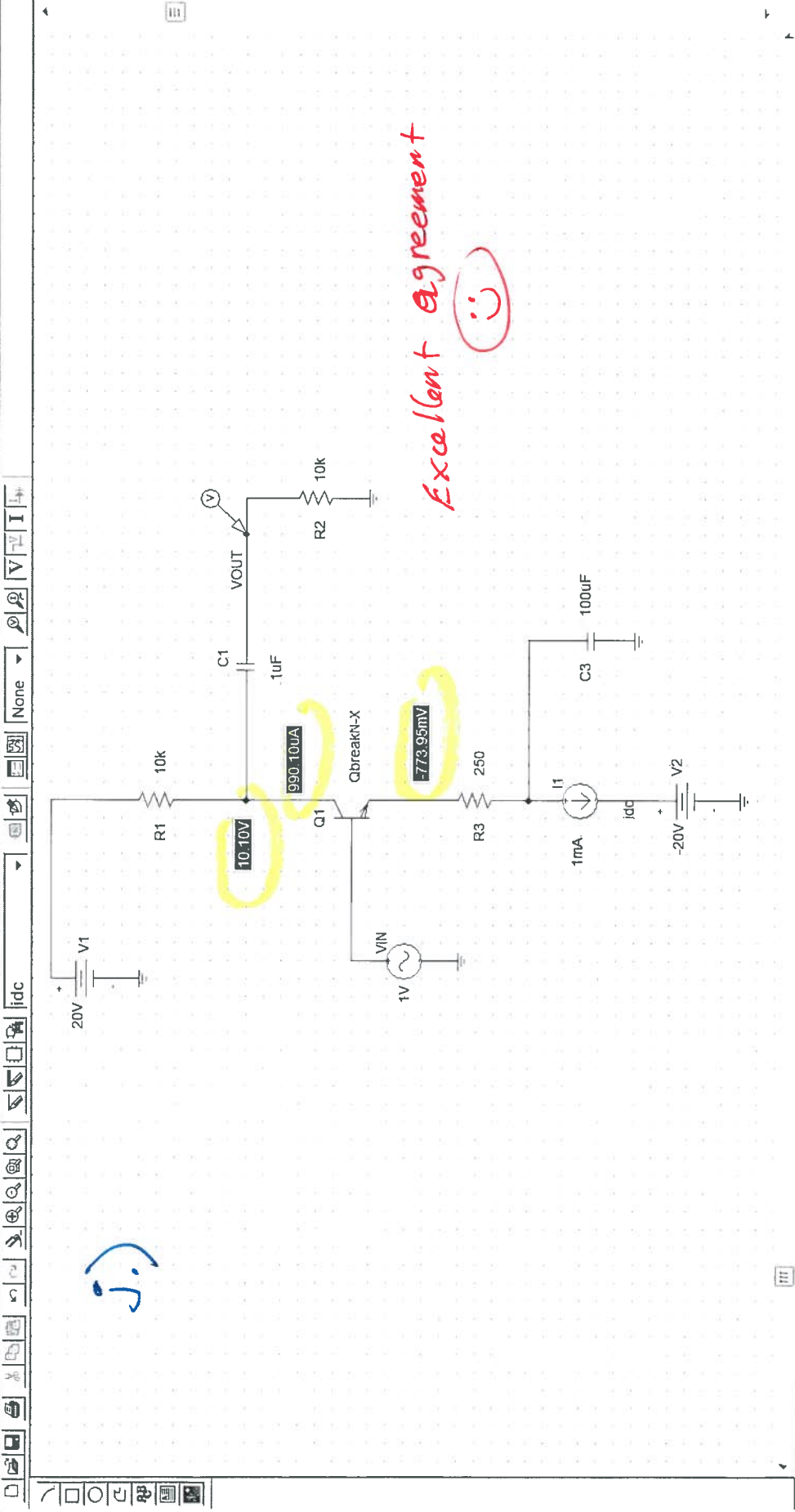i.) $f_T = \frac{g_m}{2\pi [C_{\pi} + C_{\mu}]} = 289\text{MHz}$



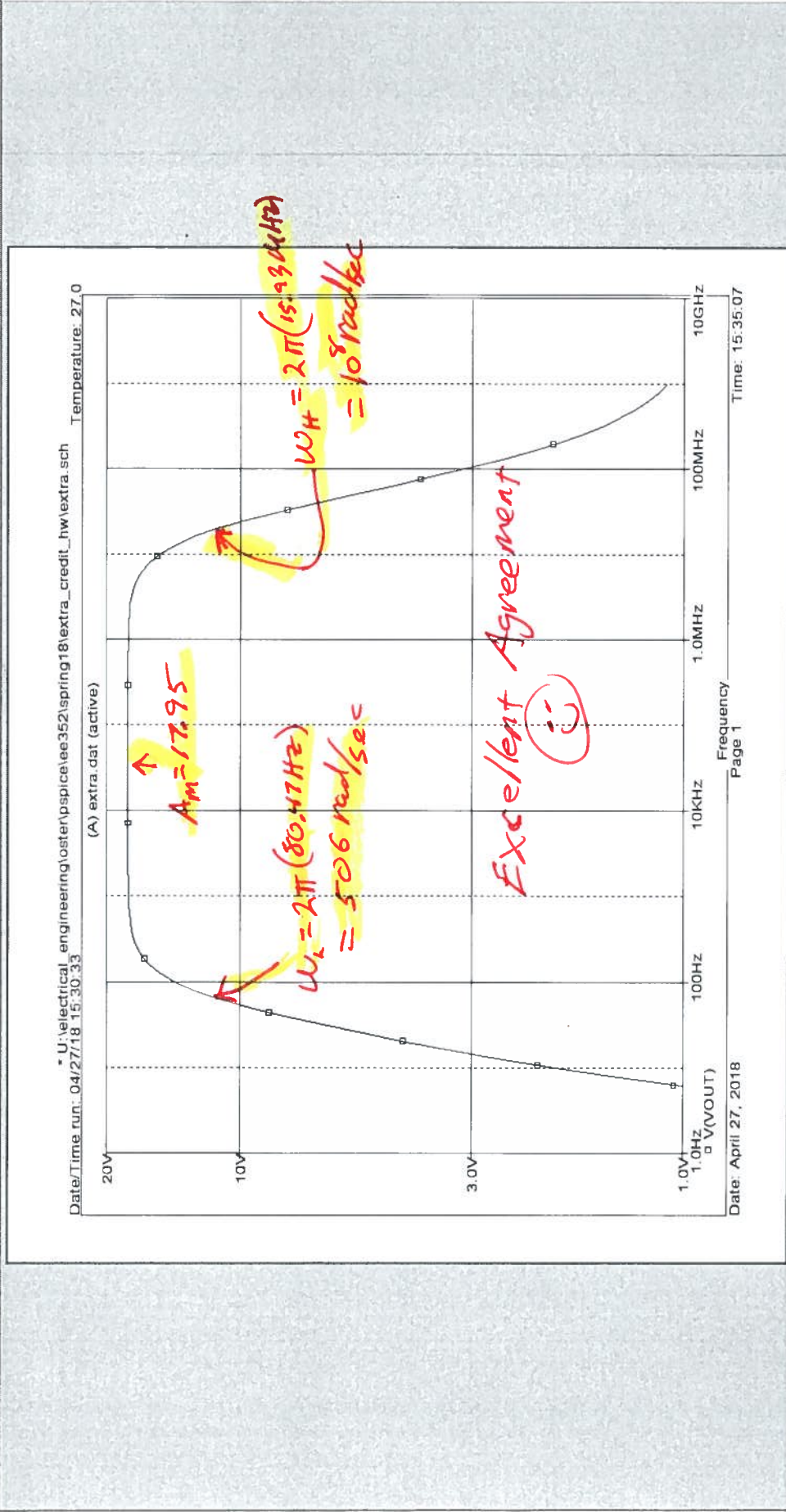

```

****      CIRCUIT DESCRIPTION
** Analysis setup **
.ac DEC 10 1 1000MEG
.OP
.LIB "U:\electrical_engineering\oster\pspice\ee352\spring18
\extra_credit_hw\extra.lib"
V_V1      $N_0001 0 20V
V_V2      $N_0002 0 -20V
I_I1      $N_0003 $N_0002 DC 1mA
R_R3      $N_0003 $N_0004 250
C_C1      $N_0005 VOUT .1uF
V_VIN     $N_0006 0 DC 0V AC 1V
C_C3      0 $N_0003 100uF
R_R1      $N_0005 $N_0001 10k
R_R2      0 VOUT 10K
Q_Q1      $N_0005 $N_0006 $N_0004 QbreakN-X
.probe
.END

```

.out file

```

****      BJT MODEL PARAMETERS
*****
*****

```

```

          QbreakN-X
          NPN
          BF 100
          MJE 0
          CJC 2.000000E-12
          MJC 0
          TF 500.000000E-12

```

```

****      BIPOLAR JUNCTION TRANSISTORS
NAME      Q_Q1
MODEL     QbreakN-X
BETADC    1.00E+02
GM        3.83E-02
RPI       2.61E+03
RO        1.00E+12
CBE       1.91E-11
CBC       2.00E-12
FT/FT2    2.88E+08

```

Hand
.04
2.5K
∞
20pF
2pF
289MHz

Excellent agreement
😊

```

JOB CONCLUDED
TOTAL JOB TIME .05

```