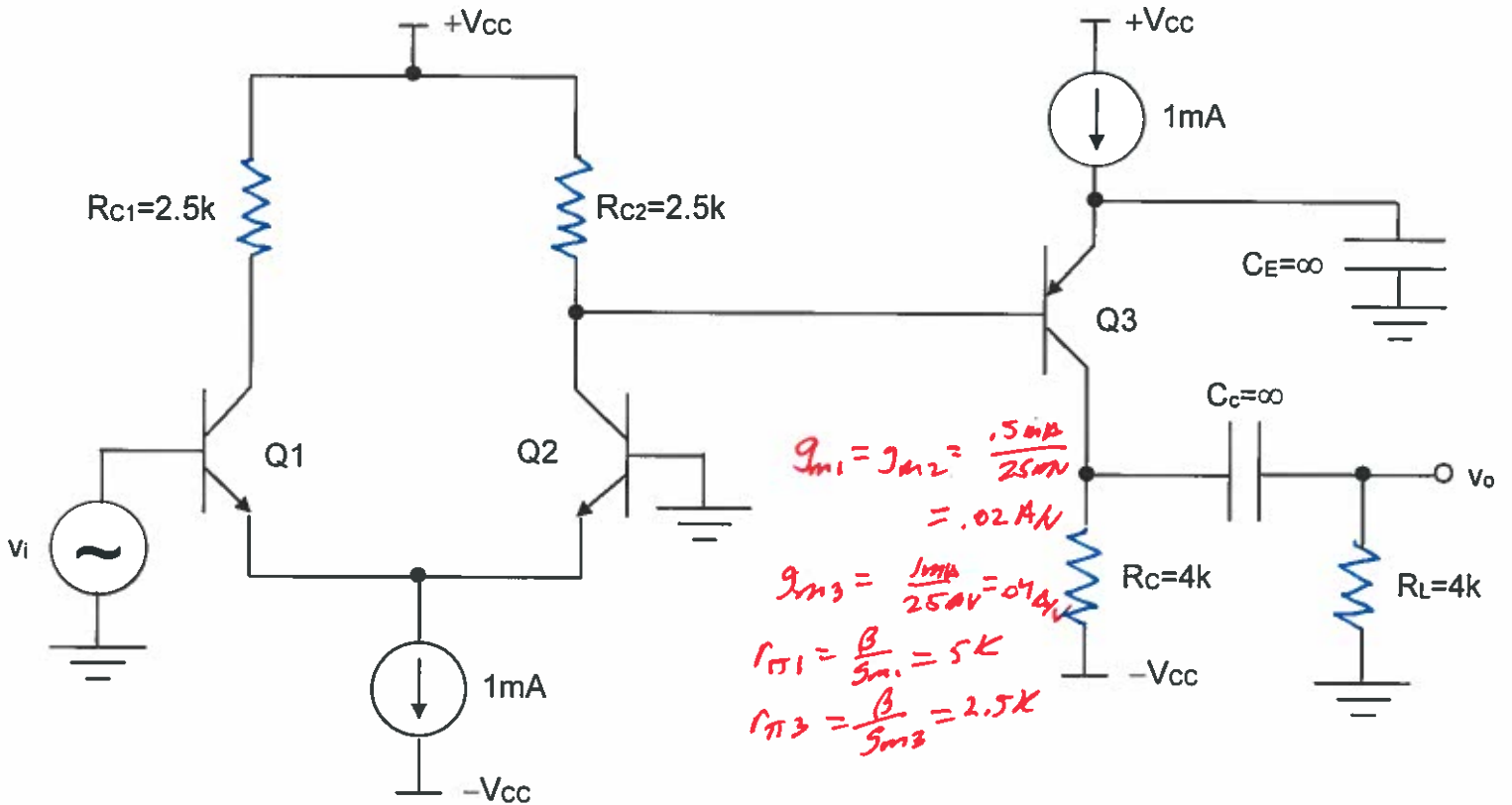


**Problem 1 (40 points):**

Consider the following amplifier comprised of a BJT Diff Amp in cascade with a BJT CE Amp driving an output load,  $R_L$ . Assume  $\beta=100$ ,  $r_o=\infty$ , and  $V_T=25\text{mV}$  for all three transistors. You may make reasonable approximations in your analysis. Note that there is no formal DC analysis required in this problem (i.e., this is a small-signal AC midband analysis).



- Calculate the overall midband gain,  $A_m=v_o/v_i$ . (Hints: First, consider the gain of each amp separately. Then multiply them together to get the overall gain. Also, notice that the  $R_{in}$  looking into the base of Q3 acts as a load,  $R_L$ , to the Diff Amp.)
- Calculate  $R_{in}$  (looking into the Q1 input).
- Calculate  $R_{out}$  (looking into  $R_c$  and before  $R_L$ ).

$$a.) A_m = A_1 \cdot A_2; \quad A_1 = \frac{g_m}{2} (R_c \parallel r_{\pi 3}) = \frac{0.02}{2} [2.5k \parallel 2.5k] = 12.5$$

$$A_2 = -g_{m3} [R_c \parallel R_L] = -0.04 [4k \parallel 4k] = -8$$


$$A_m = (12.5 / -8) = -1.5625 \text{ V/V}$$

$$b.) R_{in} = 2r_{\pi 1} = 10k$$


$$c.) R_{out} = R_c = 4k$$

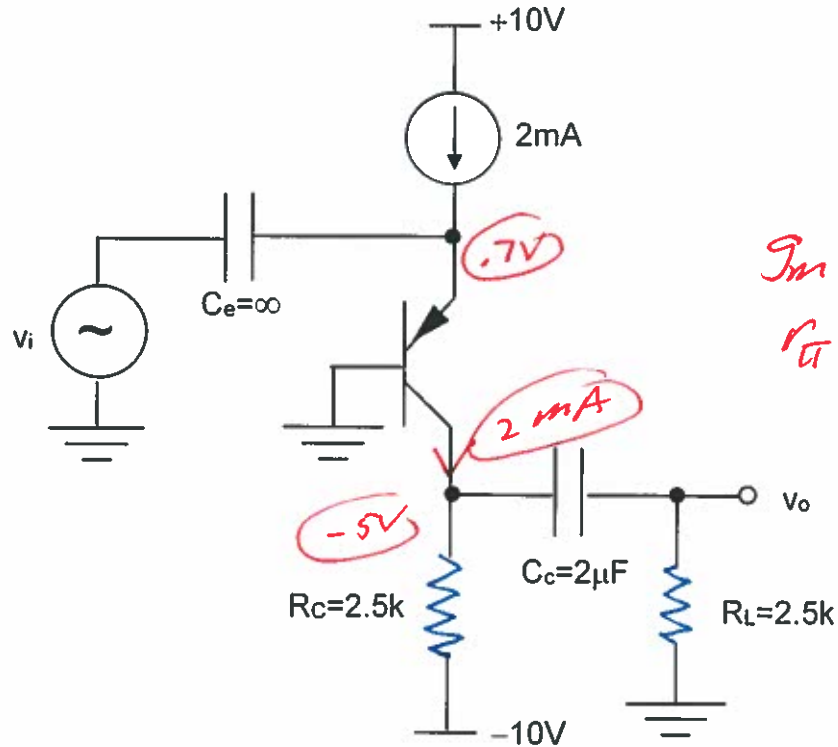**Problem 2 (60 points):**

Consider the following simple BJT CB Amplifier. Assume  $\beta=100$ ,  $V_{BE-on}=0.7V$ ,  $C_{\pi}=200pF$ ,  $C_{\mu}=80pF$ ,  $r_o=infinity$ , and  $V_T=25mV$ . You may make reasonable approximations in your analysis.




- DC Analysis: Calculate  $I_c$ ,  $V_E$  and  $V_C$ .
- AC Midband Analysis: Sketch and label the midband small-signal AC model and calculate  $A_M$ ,  $R_{in}$ , and  $R_{out}$  (looking into  $R_c$  and before  $R_L$ )
- AC Low Frequency Analysis: Sketch and label the low frequency small-signal AC model and calculate the low frequency  $\omega_L$  using SCTC's.
- AC High Frequency Analysis: Sketch and label the high frequency small-signal AC model and calculate the high frequency  $\omega_H$  using OCTC's.
- Determine  $T(s)=V_o/V_i(s)$ . Then sketch the "magnitude" Bode Plot only.  
(Hint: The form of  $T(s)$  is  $T(s) = A_M \frac{(s/\omega_L)}{(1+s/\omega_L)(1+s/\omega_H)}$ )
- Calculate the  $f_t$  of the BJT.

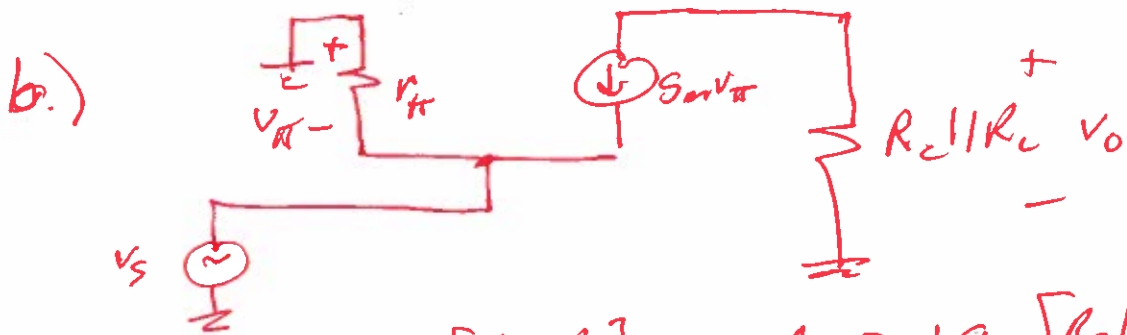

$$v_o = -g_m v_{\pi} [R_C || R_L] \Rightarrow A_m = +g_m [R_C || R_L] = +.08 [1.25K]$$

$$A_m = +100$$

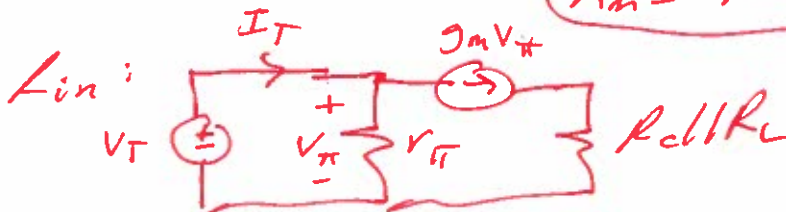


$$R_{in} = \frac{v_{\pi}}{I_T}; \quad I_T = \frac{v_{\pi}}{r_{\pi}} + g_m v_{\pi} = \frac{v_{\pi}}{r_{\pi}} [1 + \beta] = \frac{v_{\pi}}{r_{\pi}} (1 + \beta)$$

$$\therefore R_{in} = \frac{v_{\pi}}{I_T} = \frac{r_{\pi}}{1 + \beta} = \frac{1.25K}{101} = 12.4 \Omega$$


$$R_{out} = R_C = 2.5K$$

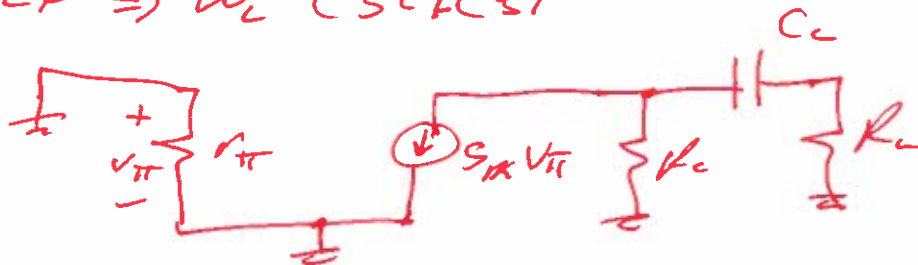c.) LF  $\Rightarrow$   $\omega_L$  (SCTCS)




$$\omega_L = \frac{1}{\tau_{C_C}} = \frac{1}{R_C C_C} = \frac{1}{(R_C + R_L) C_C} = 100 \text{ rad/sec}$$

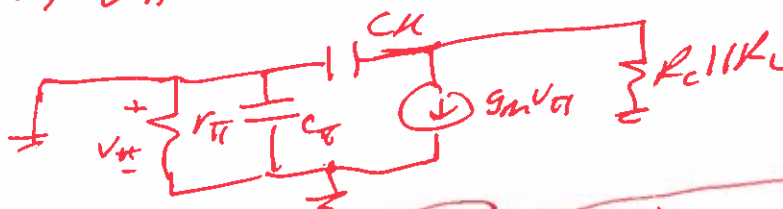d.) HF  $\Rightarrow$   $\omega_H$  (COCTCS)



$$\omega_H = \frac{1}{\tau_{C_C} + \tau_{C_{\pi}}} ; \quad \tau_{C_{\pi}} = 0 ; \quad \tau_{C_C} = (R_C || R_L) C_C = 10^{-7} \Rightarrow \omega_H = \frac{1}{\tau_{C_C}} = 10^7 \text{ rad/sec}$$
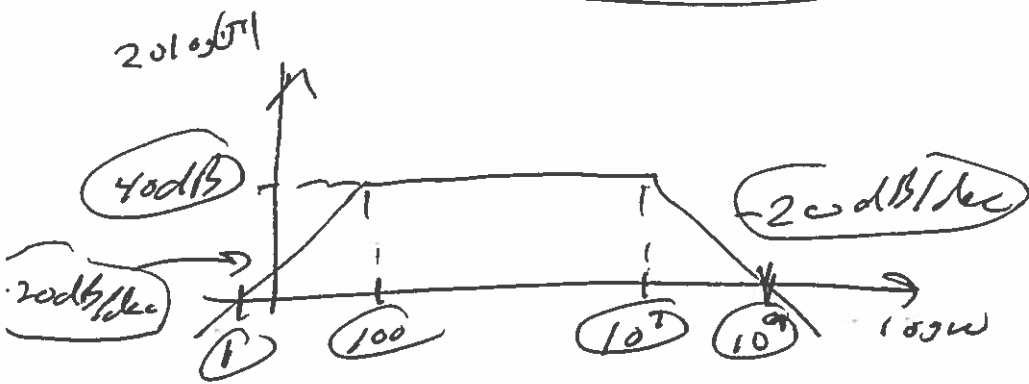
$$e.) T(s) = 100 \frac{s/100}{(1+s/100)(1+s/10^7)}$$




$$f.) f_{GT} = \frac{g_m}{2\pi [C_{\pi} + C_{\mu}]} = \frac{.68}{2\pi [280 \text{ pF}]} = 45.5 \text{ MHz}$$

**Optional Bonus Problem (10 points, no partial credit):**

Consider the following MOS Current Source/Mirror. Assume both nFET's are matched. Assume  $W_1=40\mu\text{m}$ ,  $W_2=10\mu\text{m}$ ,  $L_1=L_2=1\mu\text{m}$ , and  $I_R=100\mu\text{A}$ .

Calculate  $I_o$ .

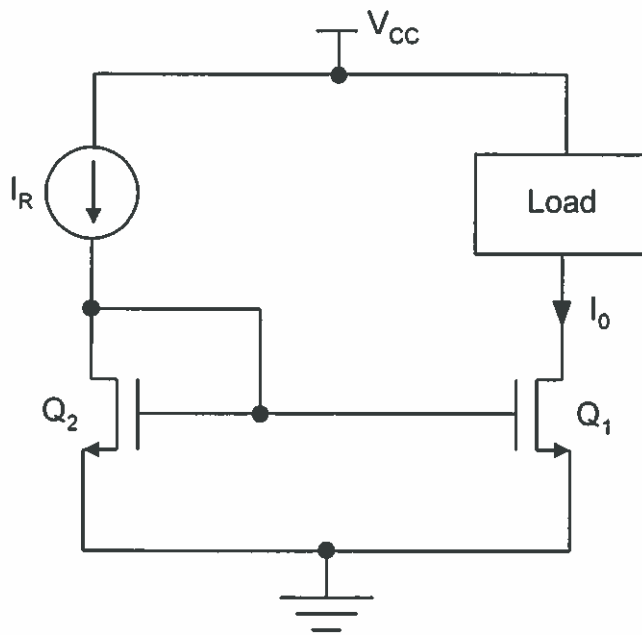

$$I_o = \frac{W_1}{W_2} I_R = \frac{40}{10} (100\mu\text{A}) = 400\mu\text{A}$$