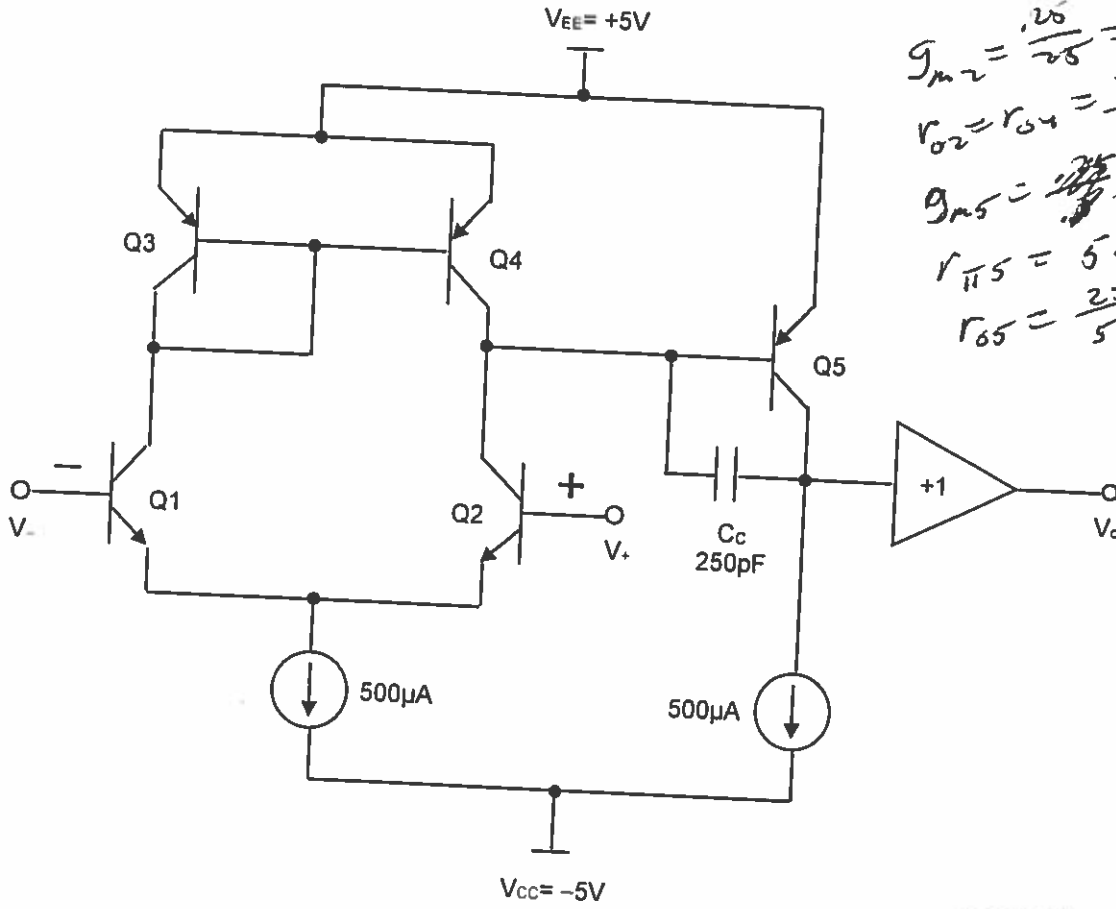


Problem 1 (20 points)

Consider the following open-loop opamp circuit. Assume the unity-gain output buffer is *ideal*. Assume $\beta_n = \beta_p = 100$, $V_{An} = V_{Ap} = 250V$, and $V_T = 25mV$. Please make reasonable approximations where appropriate.



$$g_{m2} = \frac{.25}{25} = .01$$

$$r_{o2} = r_{o4} = \frac{250}{.25m} = 1M$$

$$g_{m5} = \frac{.25}{25} = .01$$

$$r_{\pi 5} = 5K$$

$$r_{o5} = \frac{250}{500\mu} = 500K$$

- a) Calculate the ω_t of the opamp. $\omega_t = \frac{g_{m2}}{C_c} = 40M \text{ rad/sec}$
- b) Calculate the SR of the opamp. $SR = \frac{f_{cl}}{C_c} = 2V/\mu s$
- c) Calculate the A_0 of the opamp. $A_0 = g_{m2} [r_{o2} || r_{o4} || (r_{\pi 5})] g_{m5} r_{o5} = 500K \text{ V/V}$
- d) Calculate the ω_H of the opamp. $\omega_H = \frac{\omega_t}{A_0} = 80 \text{ rad/sec}$

Problem 2 (20 points)


Consider the following 2nd-order Transfer Function $T(s)$:

$$T(s) = \frac{1000}{10^{-12}s^2 + 4 \times 10^{-7}s + 1}$$

$\omega_n = 10^6$
 $\zeta = .2$

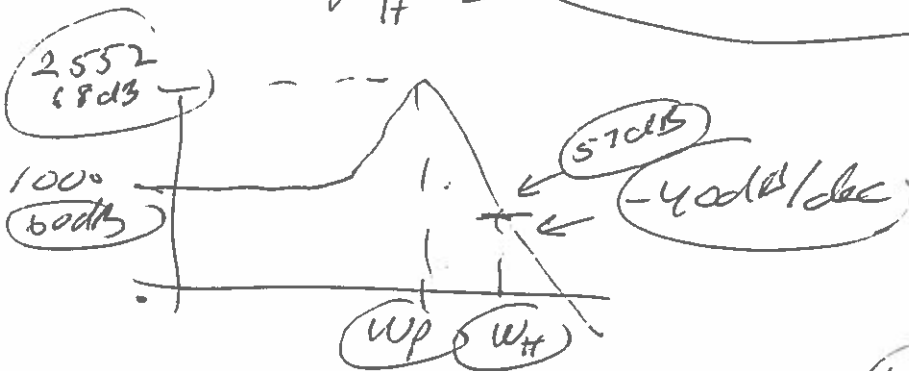- a) Using the "Calculator Sheet", calculate M_p , ω_p , and ω_H . Sketch and label the Bode Magnitude Plot.
- b) Using the "Calculator Sheet", calculate t_r , t_p and P_0 . Sketch and label the Step Response, $v_o(t)$, if $v_i(t)$ is a 0-to-1mV step.


a.) $M_p = 2.552$
 $\omega_p = 9.59 \times 10^5 \text{ rad/sec}$
 $\omega_H = 1.51 \times 10^6 \text{ rad/sec}$



b.) $t_r = 1.46 \mu s$
 $t_p = 3.2 \mu s$
 $P_0 = 1.53$



3)

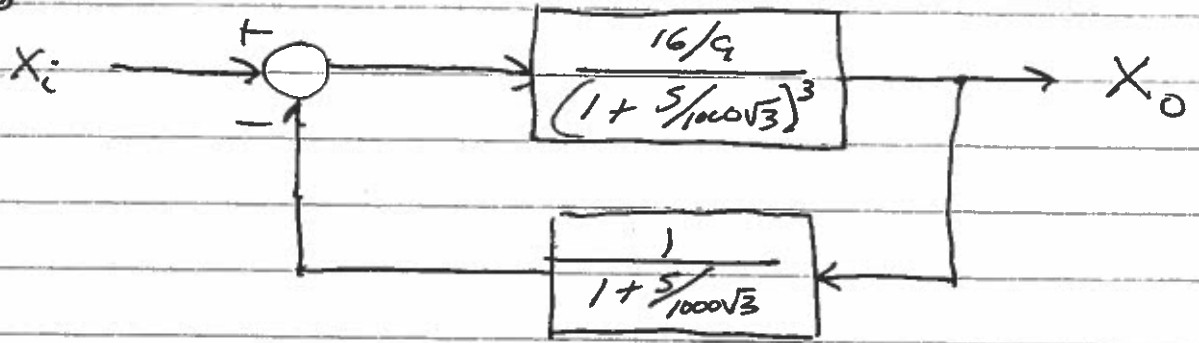

$$a.) \quad LG(s) = A(s) \beta(s) = \frac{16/9}{(1 + s/1000\sqrt{3})^4}$$

$$b.) \quad PM = 180^\circ - |\angle LG(j\omega_1)|$$

$$\angle LG(j\omega_1) = -4 \tan^{-1} \frac{\omega_1}{1000\sqrt{3}}$$

$$|LG(j\omega_1)| = 1 = \frac{16/9}{\left[1 + \left(\frac{\omega_1}{1000\sqrt{3}}\right)^2\right]^2}$$

$$1 = \frac{4/3}{1 + \frac{\omega_1^2}{3 \times 10^6}}$$

$$\frac{\omega_1^2}{3 \times 10^6} = \frac{1}{3} \Rightarrow \boxed{\omega_1 = 1000 \text{ rad/sec}}$$

$$\angle LG(j\omega_1) = -4 \tan^{-1} \frac{1000}{1000\sqrt{3}} = -4 \tan^{-1} \frac{1}{\sqrt{3}}$$

$$= (-4)(30^\circ) = -120^\circ$$

$$PM = 180^\circ - |-120^\circ| = \boxed{60^\circ}$$

$$c.) \text{GM} = 20 \log \left[\frac{1}{|LG(j\omega_{180})|} \right]$$

$$|LG(j\omega_{180})| = \frac{16/9}{\left[1 + \left(\frac{\omega_{180}}{\sqrt{3} \times 10^3} \right)^2 \right]^2}$$

$$\angle LG(j\omega_{180}) = -180^\circ = -4 + \tan^{-1} \frac{\omega_{180}}{\sqrt{3} \times 10^3}$$

$$\therefore 45^\circ = \tan^{-1} \frac{\omega_{180}}{\sqrt{3} \times 10^3}$$

$$\Rightarrow \boxed{\omega_{180} = \sqrt{3} \times 10^3 \text{ rad/sec}}$$

$$\therefore |LG(j\omega_{180})| = \frac{16/9}{(1+1)^2} = \frac{16/9}{4}$$


$$= .444$$

$$\therefore \text{GM} = 20 \log \left[\frac{1}{.444} \right]$$

$$\boxed{\text{GM} = 7.04 \text{ dB}}$$

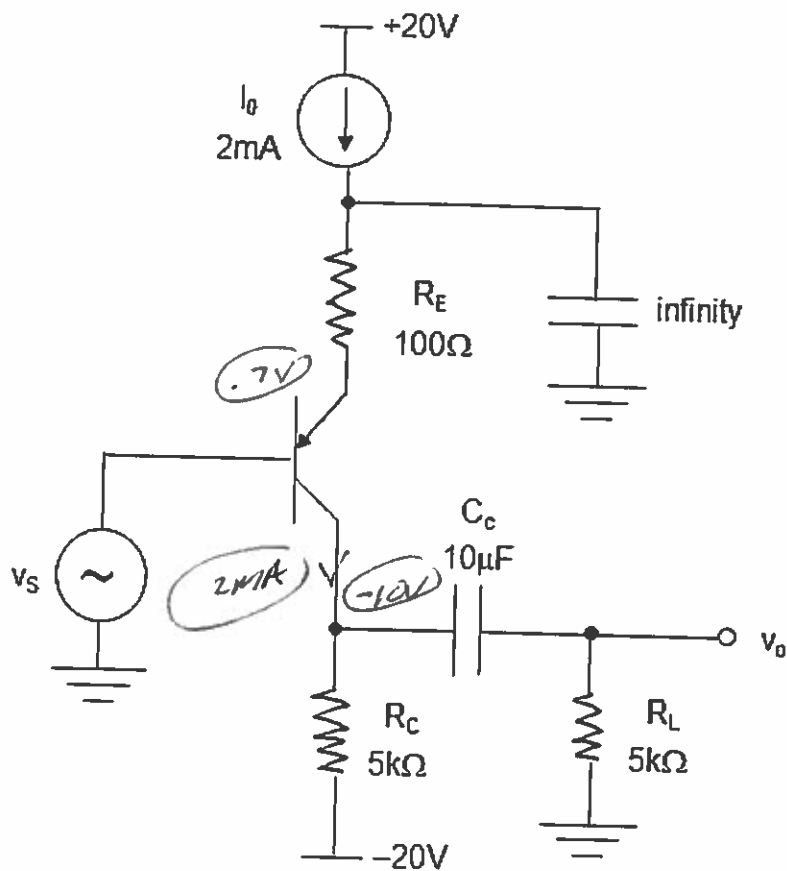
Problem 4 (20 points)

Consider the following simple BJT CE Amplifier with Emitter Degeneracy. Assume $\beta=200$, $V_{BE-on}=0.7V$, $C_{\pi}=400pF$, $C_{\mu}=40pF$, $V_T=25mV$ and $r_o=infinity$. Please make reasonable approximations where appropriate.



- DC Analysis: Calculate I_C , V_E , and V_C (Remember, please make reasonable approximations).
- Sketch and label the full SS AC model.
- Calculate A_M exactly. What happens to A_M if β goes to infinity?
- Calculate ω_L using SCTC's.
- Calculate ω_H using OCTC's. (Hint: You may assume that $\tau_{C\pi}=0$)
- Determine $T(s)$ and sketch and label the Bode Magnitude Plot for $T(s)$. (Note: Please express $T(s)$ in its correct, simplified format).

b)

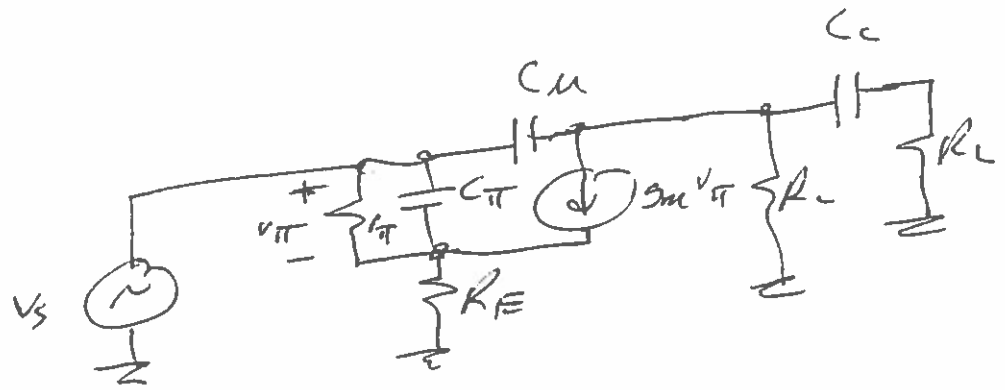

$$g_m = \frac{I_C}{V_T} = \frac{2}{25} = .08$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{200}{.08} = 2.5 \text{ k}$$

c.) $A_m = \frac{V_o}{V_s} \Rightarrow V_o = -g_m v_{\pi} [R_C || R_L]$

$$\frac{v_{\pi}}{r_{\pi}} + g_m v_{\pi} = \frac{V_s - v_{\pi}}{R_E}$$

$$v_{\pi} \left(1 + \beta + \frac{r_{\pi}}{R_E} \right) = \frac{V_s r_{\pi}}{R_E}$$

$$v_{\pi} = \frac{V_s r_{\pi}}{R_E \left(1 + \beta + \frac{r_{\pi}}{R_E} \right)}$$


$$A_m = \frac{V_o}{V_s} = - \frac{\beta [R_C || R_L]}{R_E \left(1 + \beta + \frac{r_{\pi}}{R_E} \right)} = -22.1 \text{ V/V}$$

$A_m \rightarrow -25 \text{ @ } 5 \text{ dB} \rightarrow \infty$

d.) $\omega_L = \sum \frac{1}{\tau_{Liss}} = \frac{1}{\tau_{C_C}} = \frac{1}{(R_C || R_L) C_C} = 10 \text{ rad/sec}$


e.) $\omega_H = \frac{1}{\sum \tau_{Liss}} = \frac{1}{\tau_{r_{\pi}} + \tau_{C_{C_u}}} = \frac{1}{(R_C || R_L) C_u} = 10^7 \text{ rad/sec}$

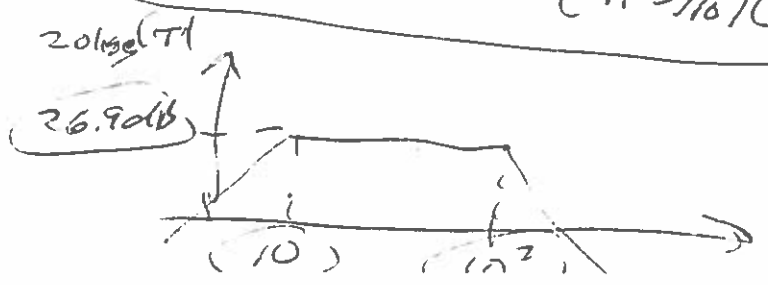f.) $T(s) = (-22.1) \frac{s/10}{(1+s/10)(1+s/10^7)}$



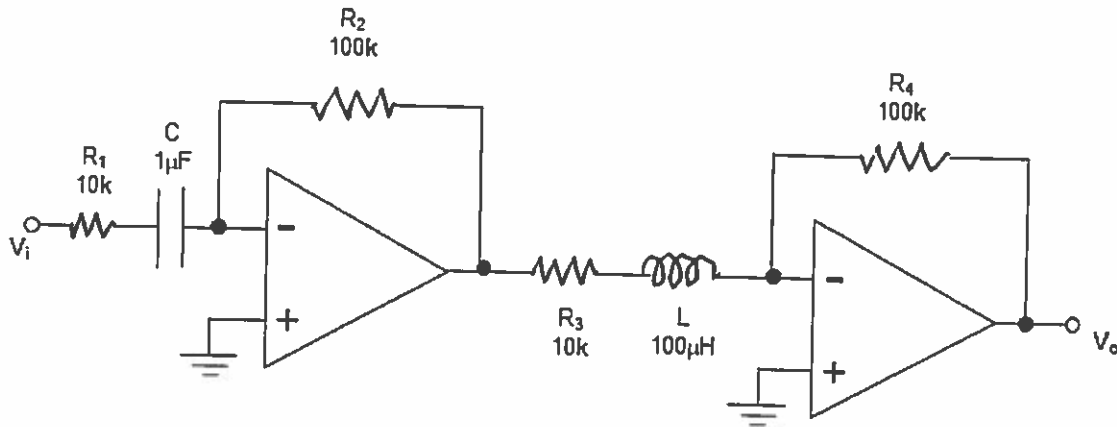Problem 5 (20 points)

Consider the following active filter comprised of two cascaded opamp amplifier circuits. Assume the opamps are *ideal*.



- Calculate the overall transfer function, $T(s) = V_o/V_i(s)$. (Hint: This is a BPF. Please express $T(s)$ in its correct, simplified format).
- Calculate the input impedance, R_{in} , of this active filter at midband frequencies.
- Calculate the output impedance, R_{out} , of this active filter.
- Sketch and label both the Bode Magnitude and Phase Plots for $T(s)$.

$$a.) \quad T_1(s) = \frac{-R_2}{R_1 + \frac{1}{Cs}} = -\frac{R_2}{R_1} \left[\frac{R_1 Cs}{1 + R_1 Cs} \right]$$



$$T_2(s) = \frac{-R_4}{R_3 + sL} = -\frac{R_4}{R_3} \left[\frac{1}{1 + s \frac{L}{R_3}} \right]$$

$$T(s) = \left[\frac{R_2 R_4}{R_3 R_3} \right] \left[\frac{R_1 Cs}{(1 + R_1 Cs)(1 + s \frac{L}{R_3})} \right]$$

$$|T(s)| = 100 \left[\frac{5/100}{(1 + 5/100s)(1 + 3/10s)} \right]$$


b.) $R_{in} = R_1 = 10k$

c.) $R_{out} = 0$

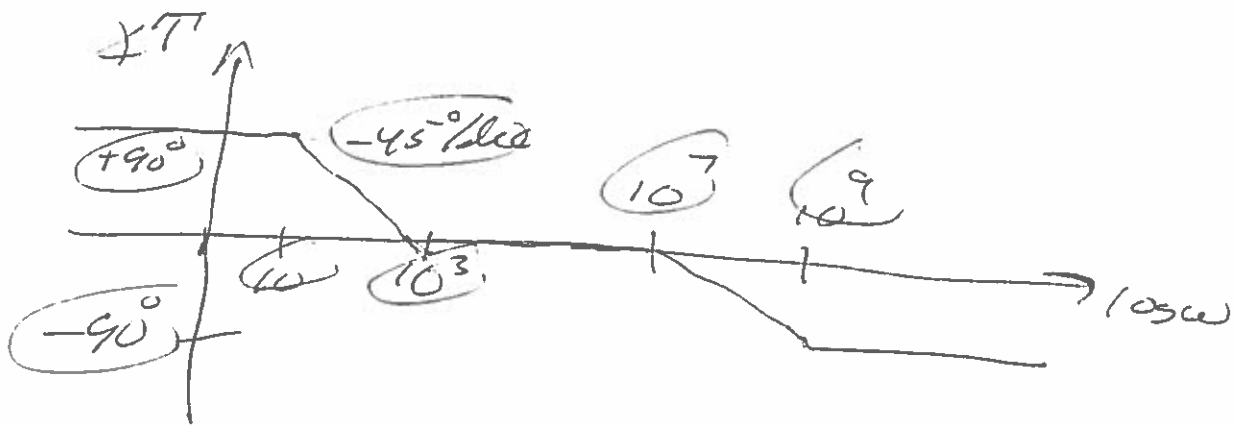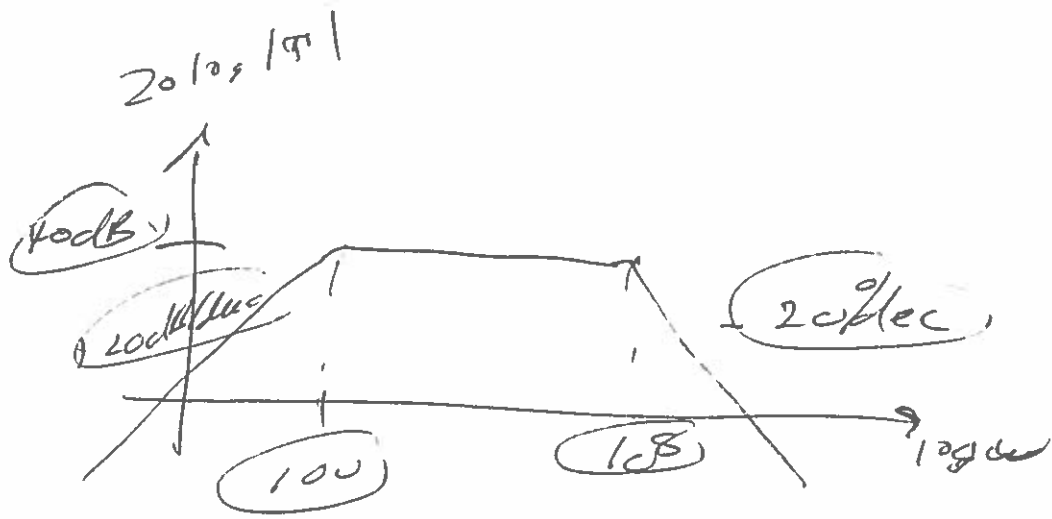

Optional Extra Credit Problem (10 points, no partial credit)

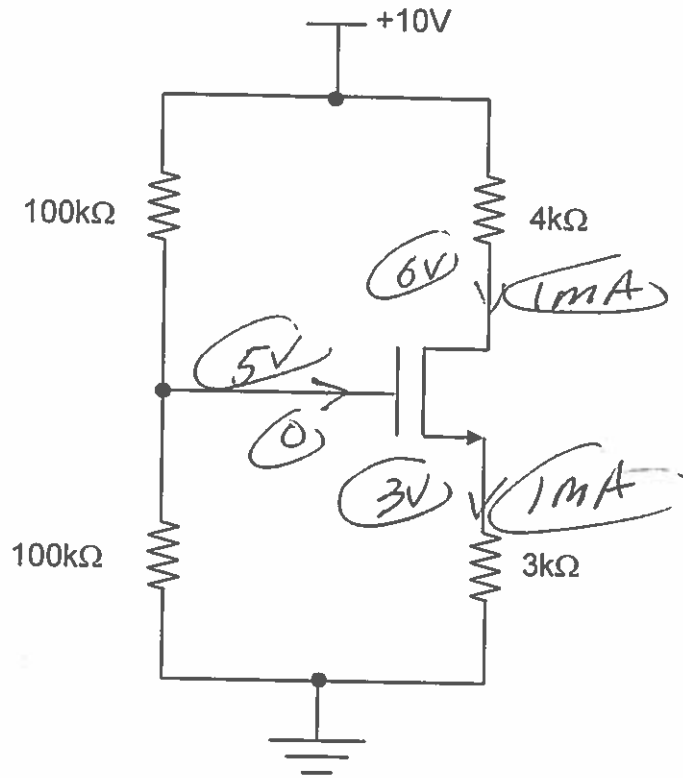Consider the following MOSFET circuit. For the nFET, assume $V_{tn}=+1V$ and $K_n=\mu_n C_{ox} W/2L=1mA/V^2$. Calculate I_D , I_S , V_G , V_S and V_D .



~~$$I_D = I_S = K_n [V_{GS} - V_{th}]^2$$

$$= 10^{-3} [(5-3) - 1]^2$$

$$= 10^{-3} A$$~~

$$I_D = K_n [V_{GS} - V_{th}]^2 = 10^{-3} [5 - \frac{V_S}{3k} - 1]^2$$

~~$$I_D = 10^{-3} [4 - \frac{V_S}{3k}]^2 = \frac{V_S}{3k}$$~~

$$3 [16 - 8V_S + V_S^2] = V_S$$

$$3V_S^2 - 25V_S + 48 = 0$$

$$V_S = \frac{25 \pm \sqrt{25^2 - (12)48}}{6} = \frac{25 \pm 7}{6} = \frac{32}{6} = 5.33V$$